



DEVELOPMENT OF A CURRENT TRANSFORMER MODEL WITH SATURATION CHARACTERISTICS

YEONG-GEUN KIM

DEPT. OF ELECTRICAL ENG., MYONGJI UNIVERSITY

USER SPOTLIGHT SERIES BY  IIRTDSTechnologies

PRESENTATION CONTENTS

❖ INTRODUCTION

❖ DEVELOPMENT OF A CT UDM (User Define Model)

- Purpose & Target CT Equivalent Circuit
- Proposed CT UDM
 - ✓ Computation of the $\phi - i$ curve from the $V_{rms} - I_{rms}$ curve
 - ✓ Dommel's network solution technique considering nonlinear circuit

❖ SIMULATION STUDIES

- Verification of the CT UDM by applying open circuit test
- Apply CT UDM to the power system

❖ CONCLUSIONS

INTRODUCTION

❖ Background

- Distorted signals caused by CT saturation results in mal-operation or operating time delay of relay
- Many utilities, including KEPCO use real-time simulators such as RTDS to perform dynamic tests of relays on CT saturation
- Some CT saturation countermeasure algorithms use nonlinear magnetization characteristic curve of CT to cope with these problems
- Need to ensure correct relay operation by detecting CT saturation or restoring the distorted signals

❖ Problem

- When V_{rms} - I_{rms} excitation curve (open circuit test data from a manufacturer) is applied to the RTDS CT model, the curve obtained from its simulation is a bit different from the applied V_{rms} - I_{rms} data

INTRODUCTION

❖ Proposed CT UDM(User Define Model) based on the modelling method of a nonlinear element suggested by Dommel

- Computation of the $\phi - i$ curve from the $V_{rms} - I_{rms}$ curve
 - ✓ L. A. N. Neves, H. W. Dommel, "On Modelling Iron Core Nonlinearities", IEEE Transactions on Power Systems, Volume 8, pp. 417 - 425, May 1993.
- Network solution technique considering nonlinear circuit
 - ✓ H. W. Dommel, "Nonlinear and time-varying elements in digital simulation of electromagnetic transients", IEEE Trans. Power App. Syst., vol. PAS-90, pp. 2561-2567, Nov./Dec. 1971.


❖ Simulation Studies

- Verification of the CT UDM and RTDS CT model by applying open circuit test
- Apply UDM to the power system model in RSCAD

DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)


Purpose & Target CT Equivalent Circuit

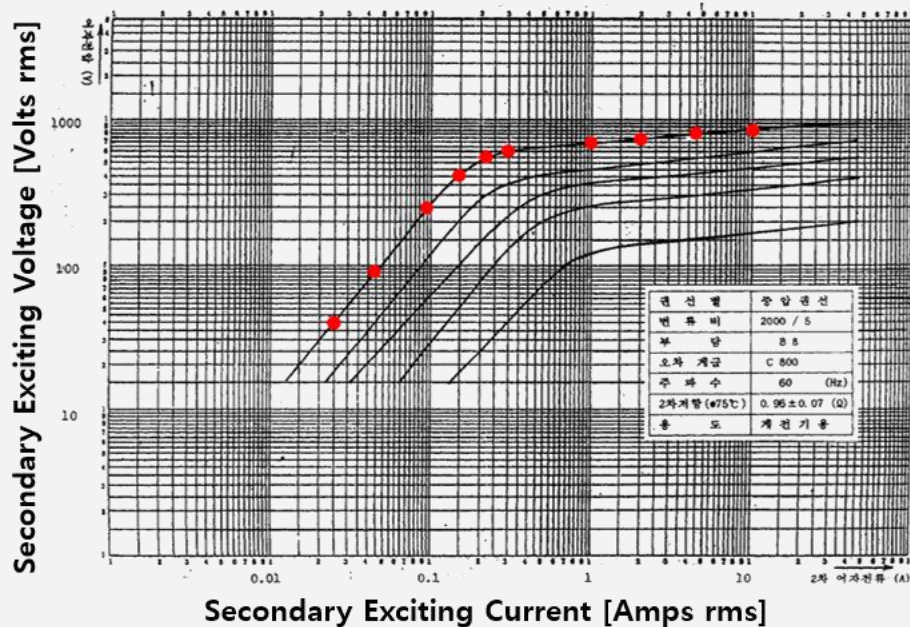- ❖ $V_{rms} - I_{rms}$ based Excitation Curve (10 points data used)
 - Linear approximation of each segment




C800 (2000:5) CT Excitation Curve

| | [I _{rms}] | [V _{rms}] |
|----------|----------------------|----------------------|
| Point 1 | 0.0129 | 40 |
| Point 2 | 0.0291 | 90 |
| Point 3 | 0.0816 | 250 |
| Point 4 | 0.134 | 400 |
| Point 5 | 0.209 | 550 |
| Point 6 | 0.283 | 600 |
| Point 7 | 0.984 | 700 |
| Point 8 | 1.98 | 750 |
| Point 9 | 4.48 | 800 |
| Point 10 | 9.98 | 850 |

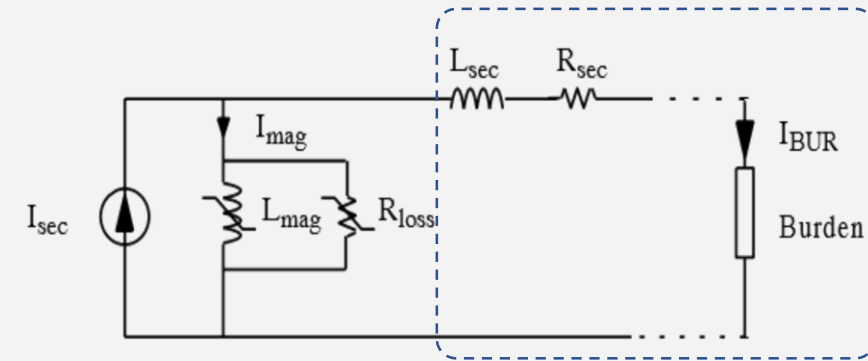

General CT Equivalent Circuit

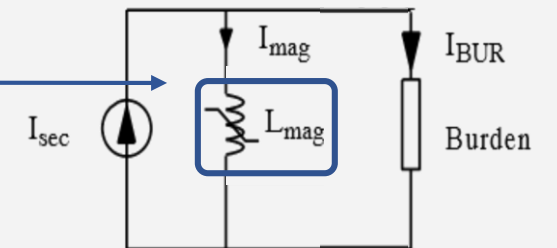


Proposed CT Equivalent Circuit

DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM

❖ Computation of the $\phi - i$ curve from the $V_{rms} - I_{rms}$ curve


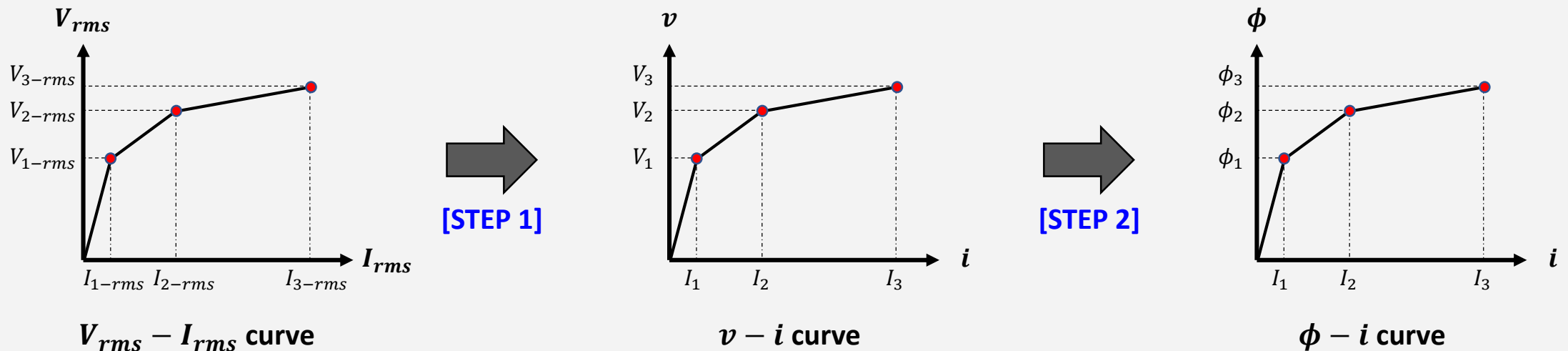
- 10 points data is used for modelling nonlinear branch (magnetizing inductance) in UDM
- An example of the computation method using 3 points is below



DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM

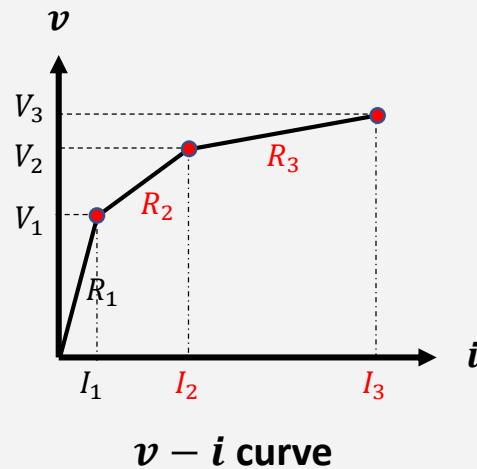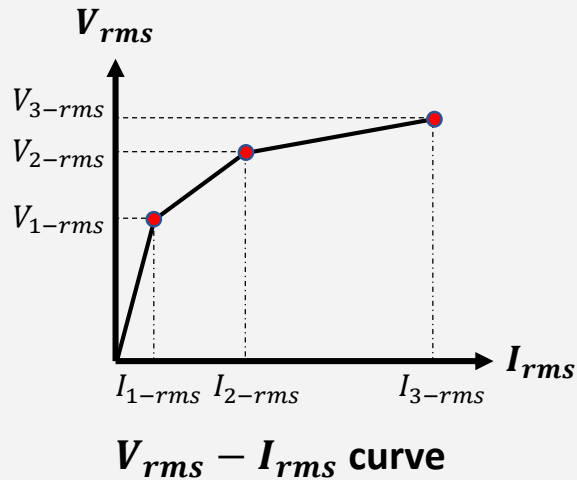❖ Computation of the $\phi - i$ curve from the $V_{rms} - I_{rms}$ curve [STEP 1]



Obtaining the points V_1, V_2, \dots, V_k on the vertical axis is simply a re-scaling procedure from rms to peak values

$$V_k = \sqrt{2}V_{k-rms}$$


Calculation of the peak current I_1 on the horizontal axis is straightforward (Since first point of V_{rms}, I_{rms} is in the linear segment)

$$I_1 = \sqrt{2}I_{1-rms}$$

DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM

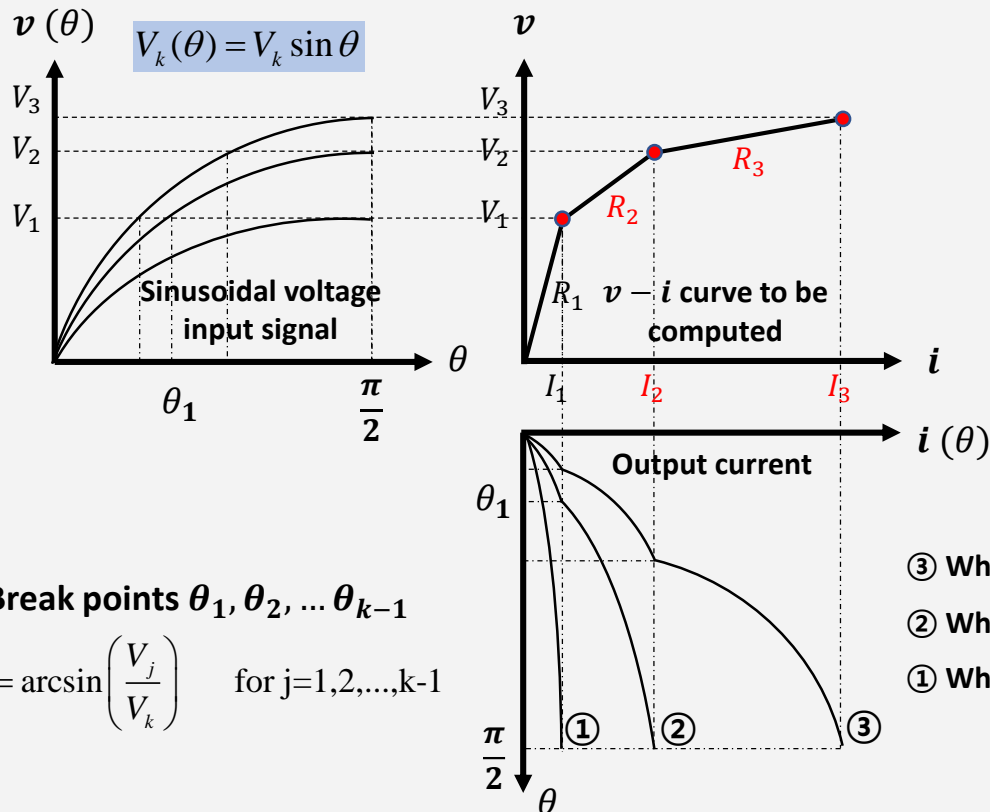❖ Computation of the $\phi - i$ curve from the $V_{rms} - I_{rms}$ curve [STEP 1]



Peak current I_k is found from the definition of the rms value ($k \geq 2$)

$$I_{rms}^2 = \frac{2}{\pi} \int_0^{\frac{\pi}{2}} i^2(\theta) d\theta$$

$$I_{k-rms}^2 = \frac{2}{\pi} \left[\int_0^{\frac{\pi}{2}} \left(\frac{V_k \sin \theta}{R_1} \right)^2 d\theta + \int_{\theta_1}^{\theta_2} \left(I_1 + \frac{V_k \sin \theta - V_1}{R_2} \right)^2 d\theta + \dots + \int_{\theta_{k-1}}^{\frac{\pi}{2}} \left(I_{k-1} + \frac{V_k \sin \theta - V_{k-1}}{R_k} \right)^2 d\theta \right]$$

Unknown value

Compute peak current I_k using R_k

$$I_k = \frac{V_k - V_{k-1}}{R_k} + I_{k-1}$$

③ When, $V_k(\theta) = V_3 \sin(\theta)$


② When, $V_k(\theta) = V_2 \sin(\theta)$

① When, $V_k(\theta) = V_1 \sin(\theta)$

DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM

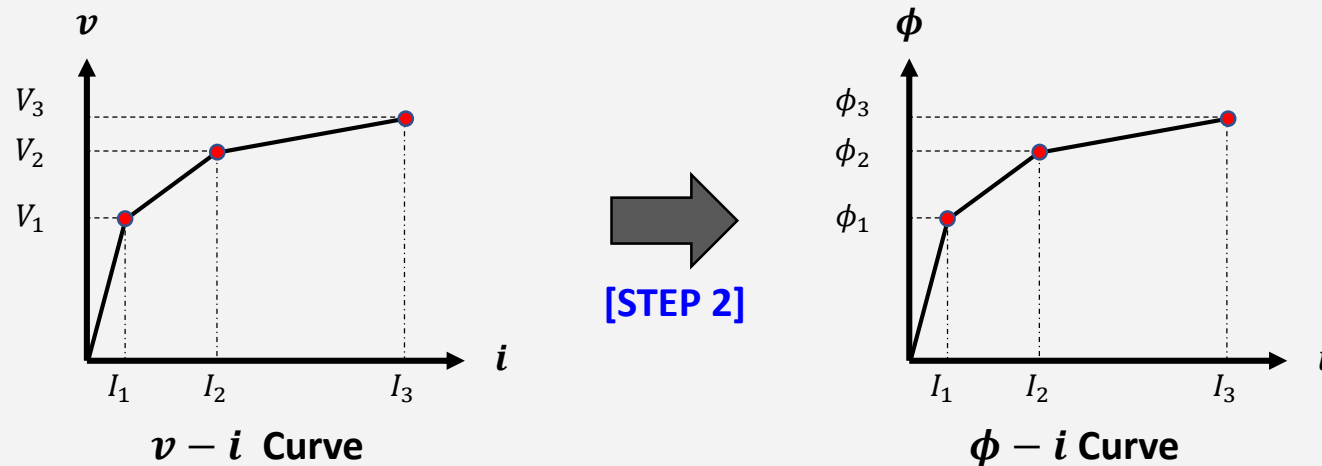
- ❖ Computation of the $\phi - i$ curve from the $V_{rms} - I_{rms}$ curve [STEP 2]



DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM

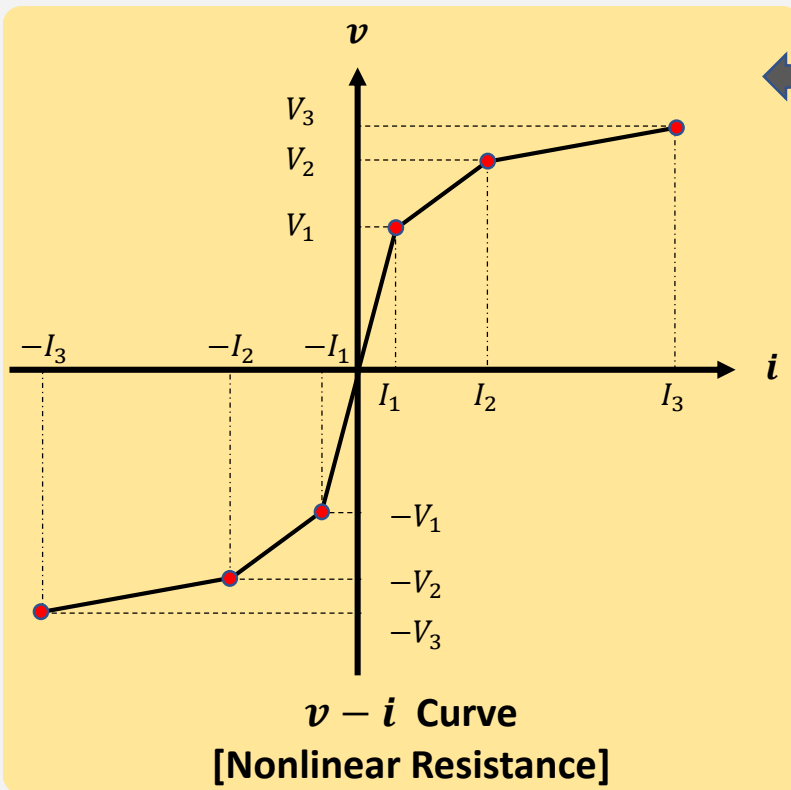❖ Computation of the $\phi - i$ curve from the $V_{rms} - I_{rms}$ curve [STEP 2]



Nonlinear resistance

$$v(t) = f(i(t))$$

Nonlinear inductance


$$\phi(t) = f(i(t))$$

$$\phi(t) = \int_{t-\Delta t}^t v(t) dt + \phi(t - \Delta t)$$

$$v(t) = \frac{2}{\Delta t} \phi(t) - v(t - \Delta t) - \frac{2}{\Delta t} \phi(t - \Delta t)$$

$$v(t) = \frac{2}{\Delta t} \phi(t) + B(t - \Delta t)$$
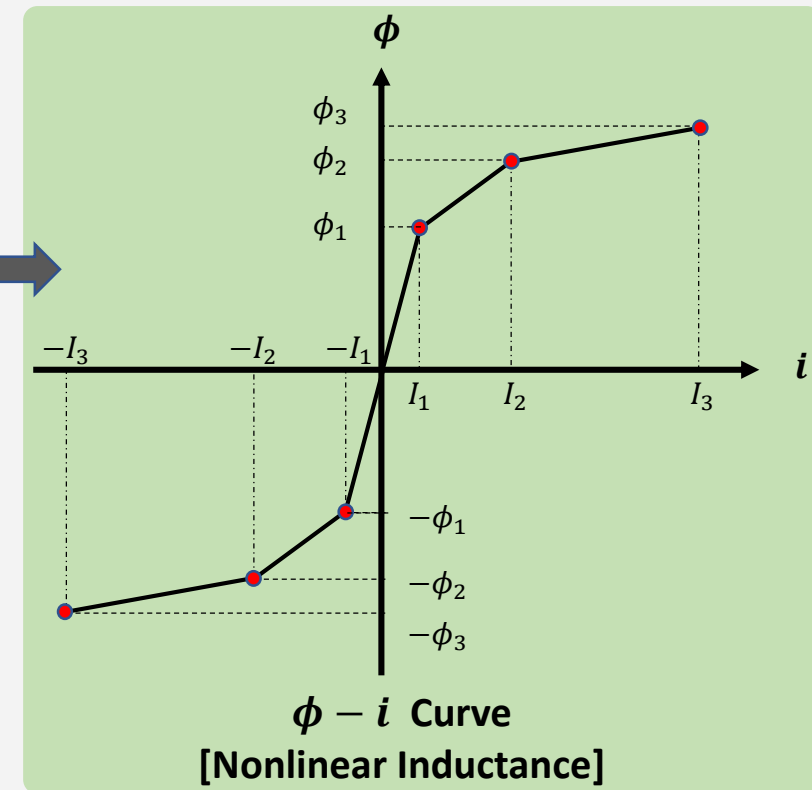
$$v(t) = \frac{2}{\Delta t} f(i(t)) + B(t - \Delta t)$$




DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)


Proposed CT UDM

❖ Network solution technique considering nonlinear circuit

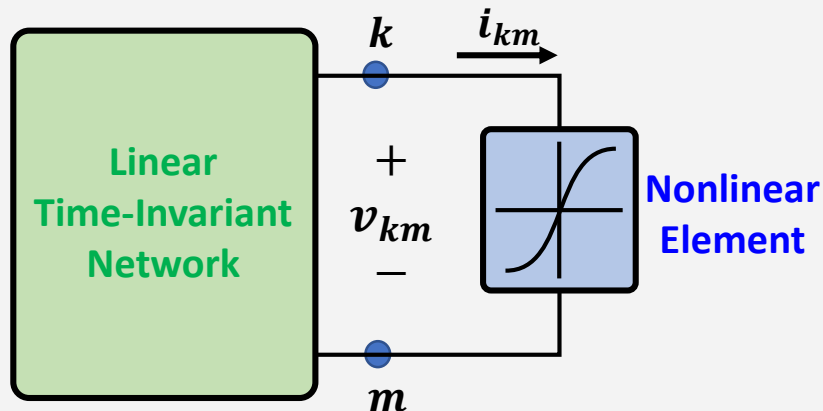- Compensation method can be applied if there is only one nonlinear element in the circuit
- Nonlinear element is replaced by a current source i_{km}



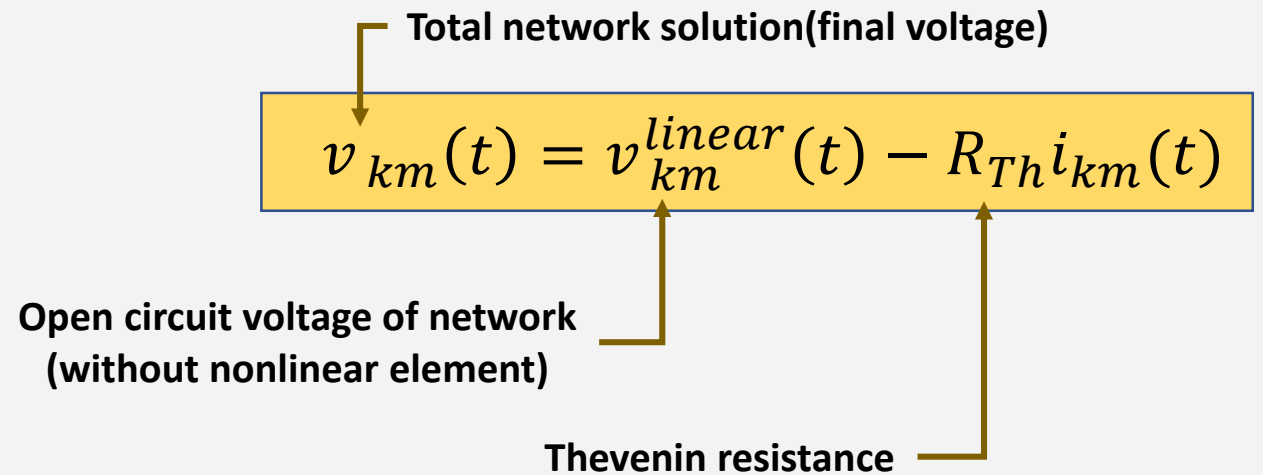Linear network including only one nonlinear element




DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM

❖ Network solution technique considering nonlinear circuit

The solution process in each time step

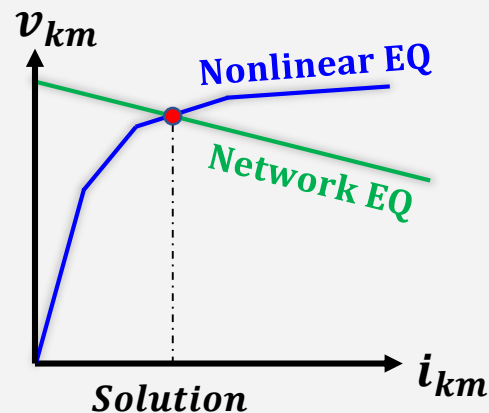- ① Compute node voltage without nonlinear element
- ② Solve the two scalar equations Network Equation and Nonlinear Equation simultaneously for i_{km}
- ③ Find the final voltage solution by super-imposing the response to the current source i_{km}



Simultaneous solution of two equations

Network Equation

$$v_{km}(t) = v_{km}^{linear}(t) - R_{Th} i_{km}(t)$$

Nonlinear Equation

$$v_{km}(t) = \frac{2}{\Delta t} f(i_{km}(t)) + B(t - \Delta t)$$


DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM



❖ Network solution technique considering nonlinear circuit

The solution process in each time step

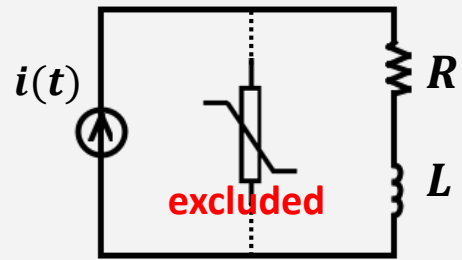
① Compute node voltage without nonlinear element



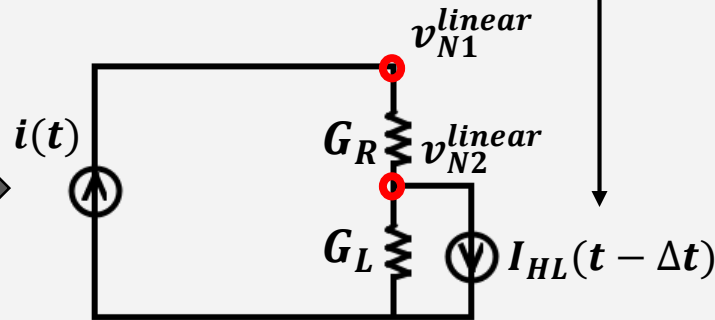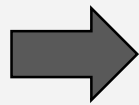Proposed CT Equivalent Circuit without nonlinear element



Dommel Equivalent Circuit

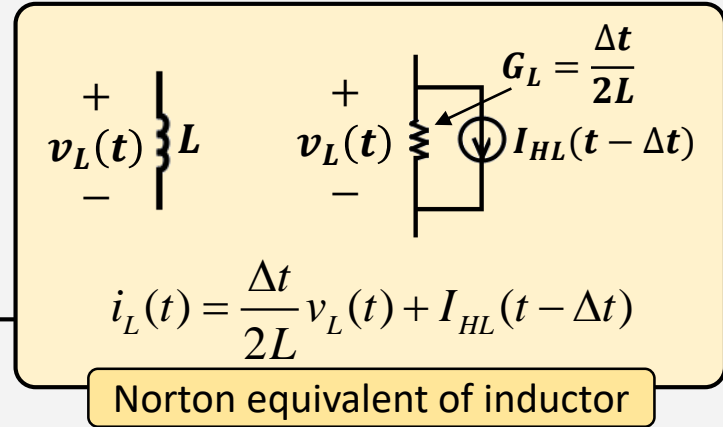

$$\begin{bmatrix} v_{N1}^{linear}(t) \\ v_{N2}^{linear}(t) \end{bmatrix} = \begin{bmatrix} G_R & -G_R \\ -G_R & G_R + G_L \end{bmatrix}^{-1} \begin{bmatrix} i(t) \\ -I_{HL}(t - \Delta t) \end{bmatrix}$$

Vector of nodal voltages Conductance matrix Vector of external current sources

Nodal equation


DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM

❖ Network solution technique considering nonlinear circuit

The solution process in each time step

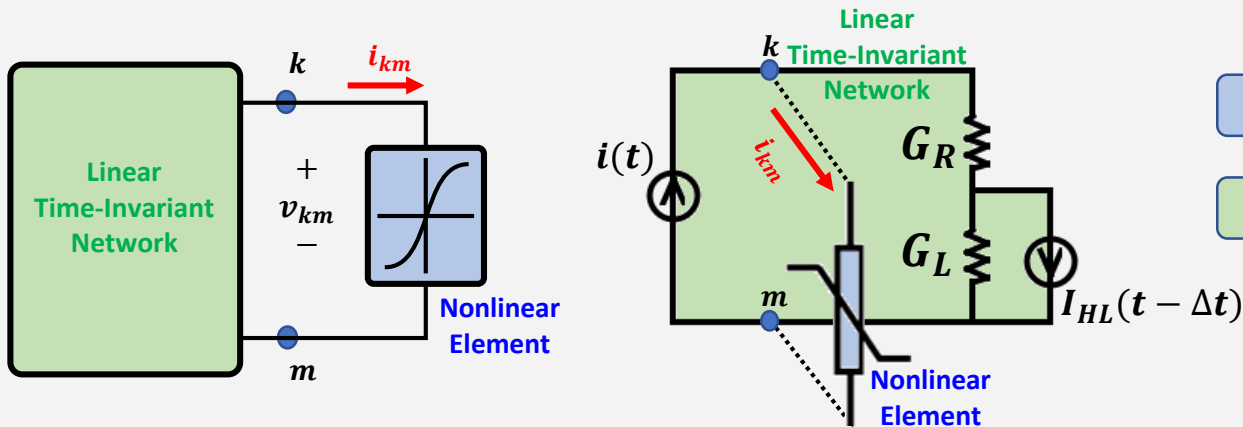- ② Solve the two scalar equations Network Equation and Nonlinear Equation simultaneously for i_{km}
- ③ Find the final voltage solution by super-imposing the response to the current source i_{km}



Linear network including only one nonlinear element

$$\begin{aligned}
 \text{Nonlinear Equation} &\rightarrow v_{km}(t) = \frac{2}{\Delta t} f(i_{km}(t)) + B(t - \Delta t) \\
 \text{Network Equation} &\rightarrow v_{km}(t) = \underbrace{v_{km}^{linear}(t)}_{\text{Open circuit voltage of network}} - \underbrace{R_{Th}}_{\text{Thevenin resistance}} i_{km}(t)
 \end{aligned}$$

Final voltage

DEVELOPMENT OF A CT UDM (USER DEFINE MODEL)

Proposed CT UDM

❖ CT UDM & model parameters



Current_Transformer.def

BURDEN **Vrms Irms DATA** SIGNAL NAMES

MAIN DATA PROCESSOR ASSIGNMENT TRANSFORMER DATA

| Name | Description | Value | Unit | Min | Max |
|-------|-------------|-------|------|-----|-----|
| Vrms1 | | 40.0 | | 0.0 | |
| Irms1 | | 0.0 | | 0.0 | |
| Vrms2 | | 90.0 | | 0.0 | |
| Irms2 | | 0.0 | | 0.0 | |
| Vrms3 | | 250.0 | | 0.0 | |
| Irms3 | | 0.0 | | 0.0 | |
| Vrms4 | | 400.0 | | 0.0 | |
| Irms4 | | 0.0 | | 0.0 | |
| Vrms5 | | 550.0 | | 0.0 | |
| Irms5 | | 0.0 | | 0.0 | |
| Vrms6 | | 600.0 | | 0.0 | |

Update Cancel Cancel All

Current_Transformer.def

BURDEN Vrms Irms DATA SIGNAL NAMES

MAIN DATA PROCESSOR ASSIGNMENT TRANSFORMER DATA

| Name | Description | Value | Unit | Min | Max |
|------|--------------------------|-------|------|------|-----|
| Rbi | Burden series resistance | 1 | Ohms | 1e-9 | |
| Lbi | Burden series inductance | 1e-9 | H | 1e-9 | |

Current_Transformer.def

BURDEN Vrms Irms DATA **SIGNAL NAMES**

MAIN DATA PROCESSOR ASSIGNMENT TRANSFORMER DATA


| Name | Description | Value | Unit | Min | Max |
|------|------------------------------|----------|------|-----|-----|
| Isec | Total Secondary Current Name | Isec_UDM | | | |
| Ibur | Burden Current Name | Ibur_UDM | | | |
| Imag | Magnetizing Current Name | Imag_UDM | | | |
| Flux | Flux Name | Flux_UDM | | | |
| Vbur | Burden Voltage Name | Vbur_UDM | | | |

SIMULATION STUDIES

Verification of the CT UDM by applying open circuit test

❖ Simulation Conditions

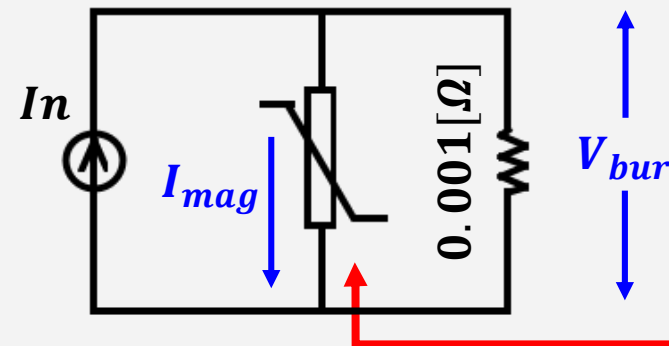- Compared Models
 - ✓ CT UDM
 - ✓ RTDS CT model
- Input Signal
 - ✓ Sinusoidal current



Proposed CT Equivalent Circuit

| | [Irms] | [Vrms] |
|----------|----------|----------|
| Point 1 | 0.0129 | 40 |
| Point 2 | 0.0291 | 90 |
| Point 3 | 0.0816 | 250 |
| Point 4 | 0.134 | 400 |
| Point 5 | 0.209 | 550 |
| Point 6 | 0.283 | 600 |
| Point 7 | 0.984 | 700 |
| Point 8 | 1.98 | 750 |
| Point 9 | 4.48 | 800 |
| Point 10 | 9.98 | 850 |

SIMULATION STUDIES

Verification of the CT UDM by applying open circuit test


① Using RTDS CT Model

- Input Saturation Characteristics Data Types

- 1) Physical Core Data
- 2) B-H Characteristic Data
- 3) **Vrms-Irms Characteristic Data**




RTDS CT Model

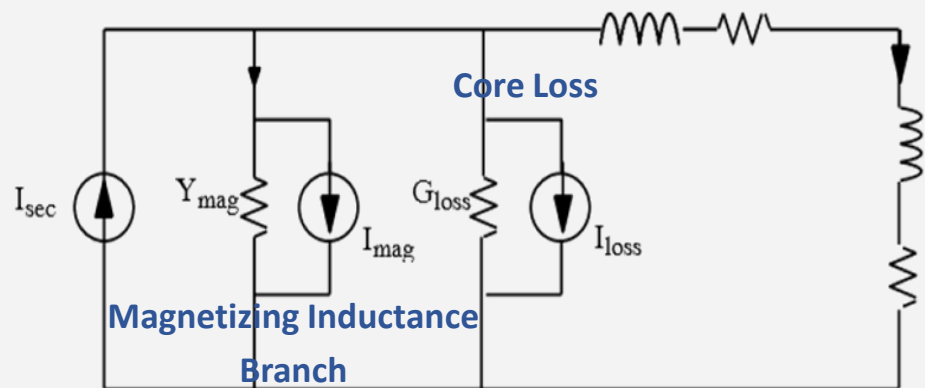

RTDS CT Equivalent Circuit

② ~~Using RTDS Saturable Reactor Model~~

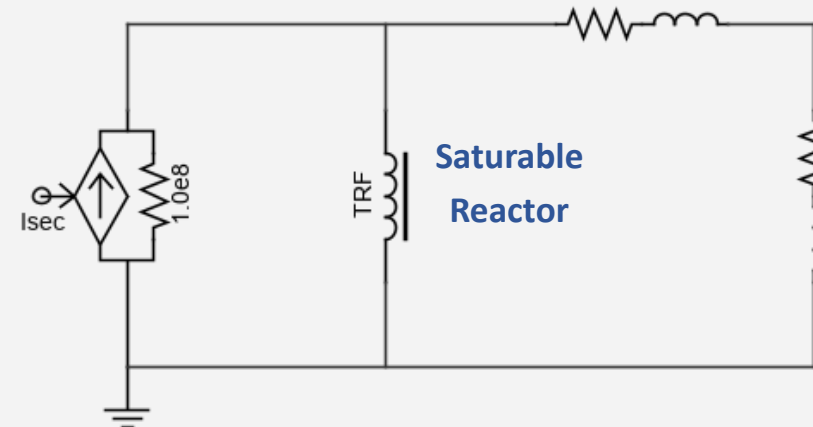- Construct a CT equivalent circuit using Saturable Reactor Model
- Input Saturation Characteristics Data
 - ✓ Linear Inductance, Knee-point Voltage, Air Core Inductance




CT Equivalent Circuit using RTDS Saturable Reactor

SIMULATION STUDIES



Verification of the CT UDM by applying open circuit test

❖ Ignore Core Loss, Secondary Resistance and Leakage Reactance

RTDS CT Model

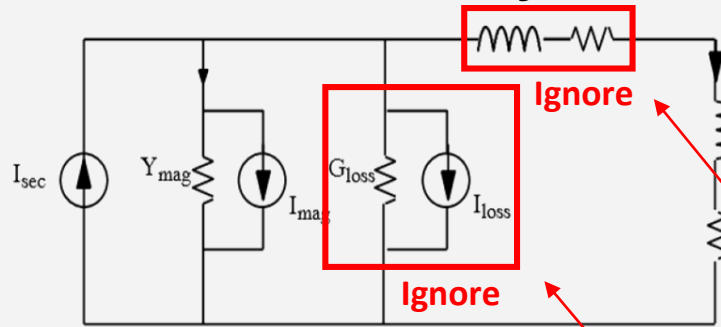RTDS CT Equivalent Circuit

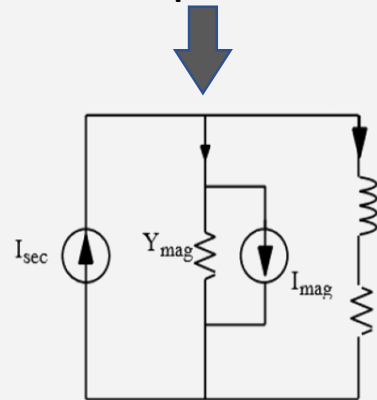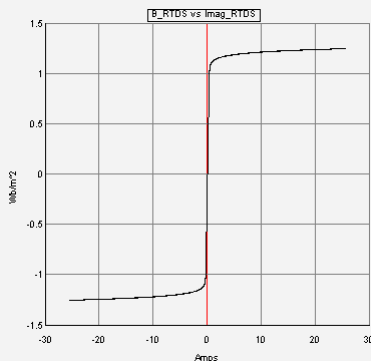

Proposed CT Equivalent Circuit

| V1,I1 ... V10,I10 | | P-LOSS DATA | | MONITORING | | SIGNAL NAMES | |
|-------------------|---------------------------|----------------------|------|------------------|-----|--------------|--|
| MAIN DATA | | PROCESSOR ASSIGNMENT | | TRANSFORMER DATA | | BURDEN | |
| Name | Description | Value | Unit | Min | Max | | |
| Rs | Secondary Side Resistance | 0.0 | Ohms | 0.0 | | | |
| Ls | Secondary Side Inductance | 0.0 | H | 0.0 | | | |
| Ratio | Turns ratio | 1 | | 0 | | | |

| V1,I1 ... V10,I10 | | P-LOSS DATA | | MONITORING | | SIGNAL NAMES | |
|-------------------|-------------|----------------------|------|------------------|-----|--------------|--|
| MAIN DATA | | PROCESSOR ASSIGNMENT | | TRANSFORMER DATA | | BURDEN | |
| Name | Description | Value | Unit | Min | Max | | |
| LoopW | Loop Width | 0 | % | 0 | 100 | | |




RTDS CT Parameters Menu

SIMULATION STUDIES




Verification of the CT UDM by applying open circuit test

❖ Burden voltage of 850 [rms volts]

CT UDM

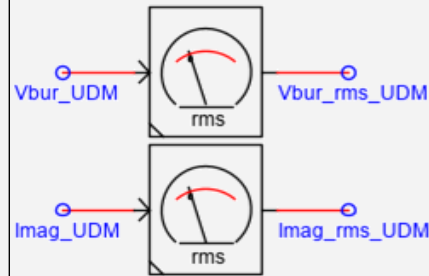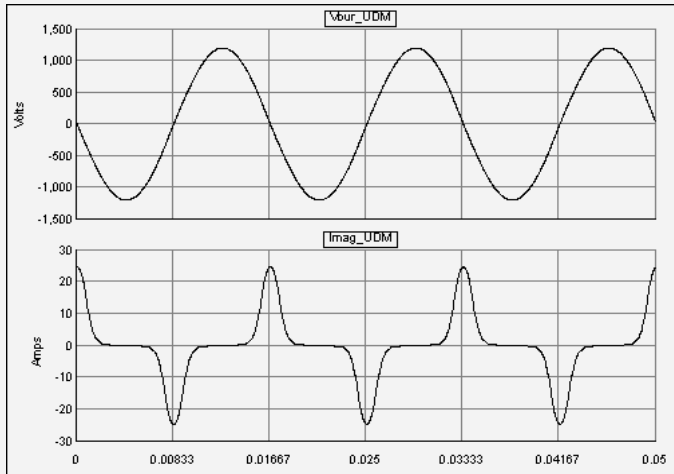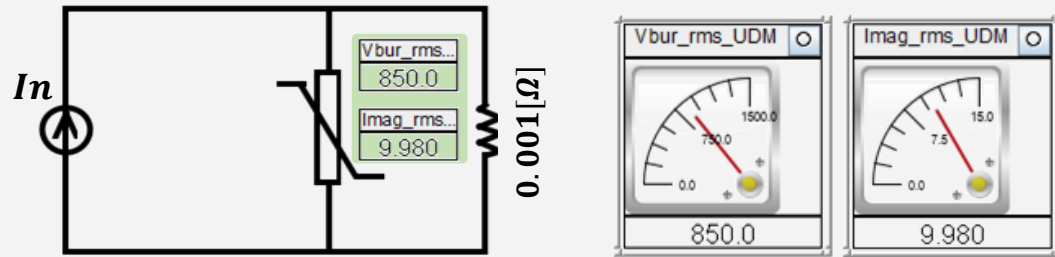




RTDS CT

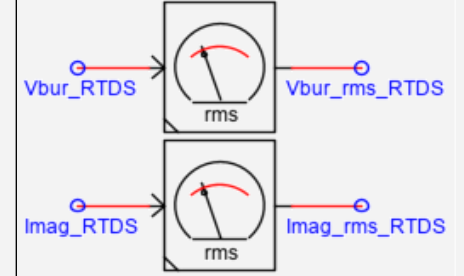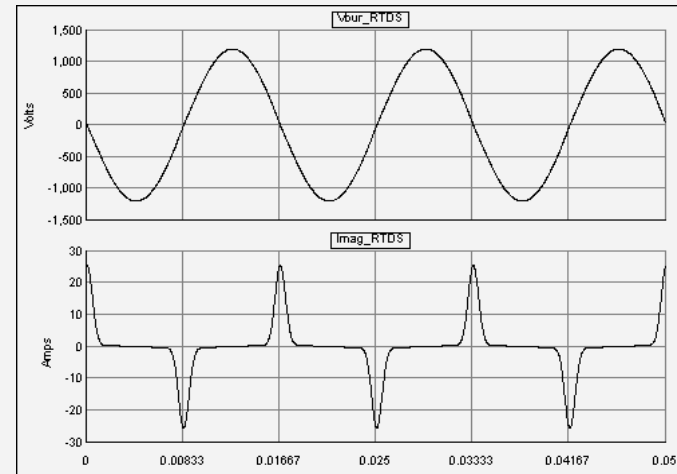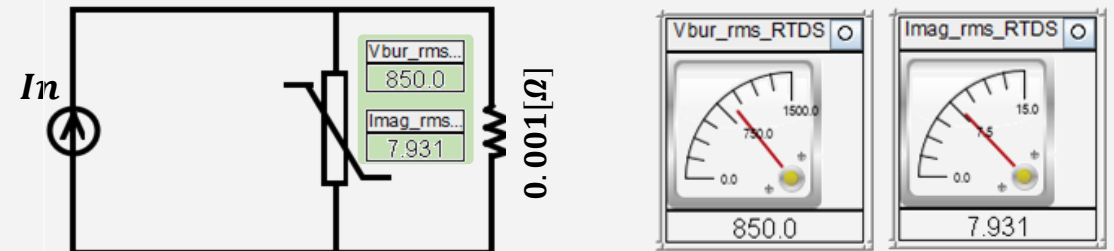

SIMULATION STUDIES

Verification of the CT UDM by applying open circuit test

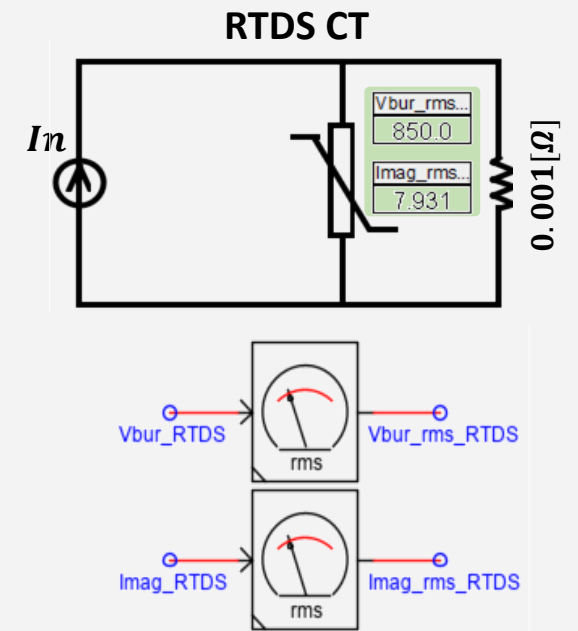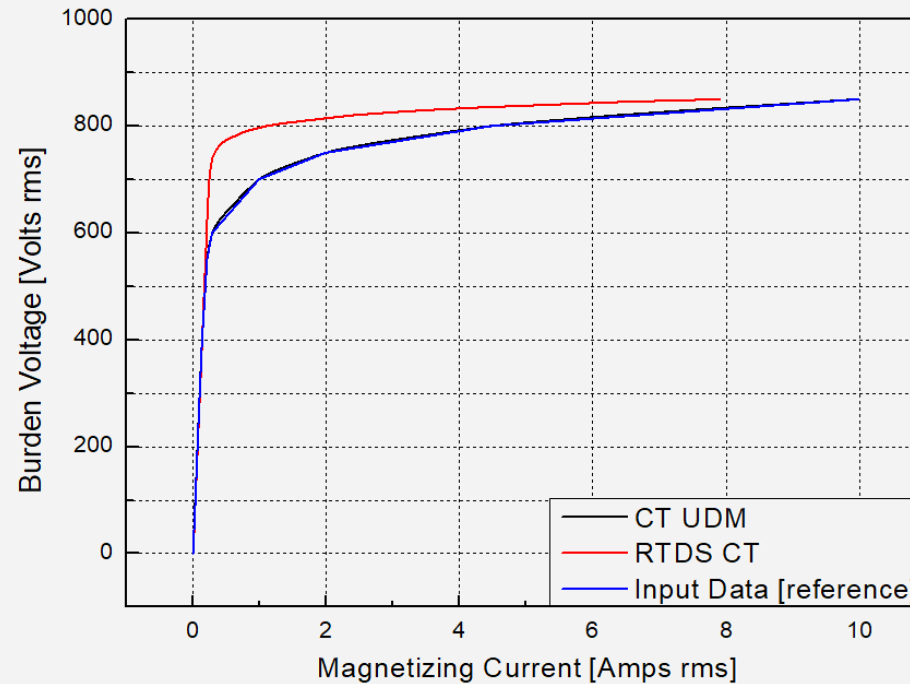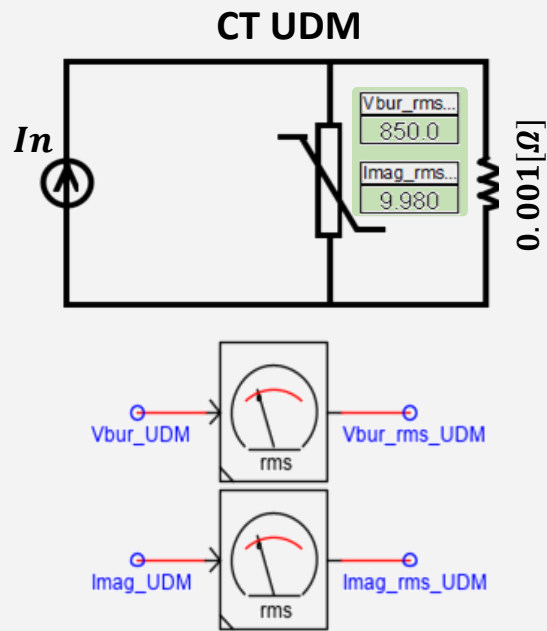- ❖ Change burden voltage from 0 to 850 [rms volts] by using script




Test results

SIMULATION STUDIES

Apply CT UDM to the power system



❖ 154 - 22.9kV Power system

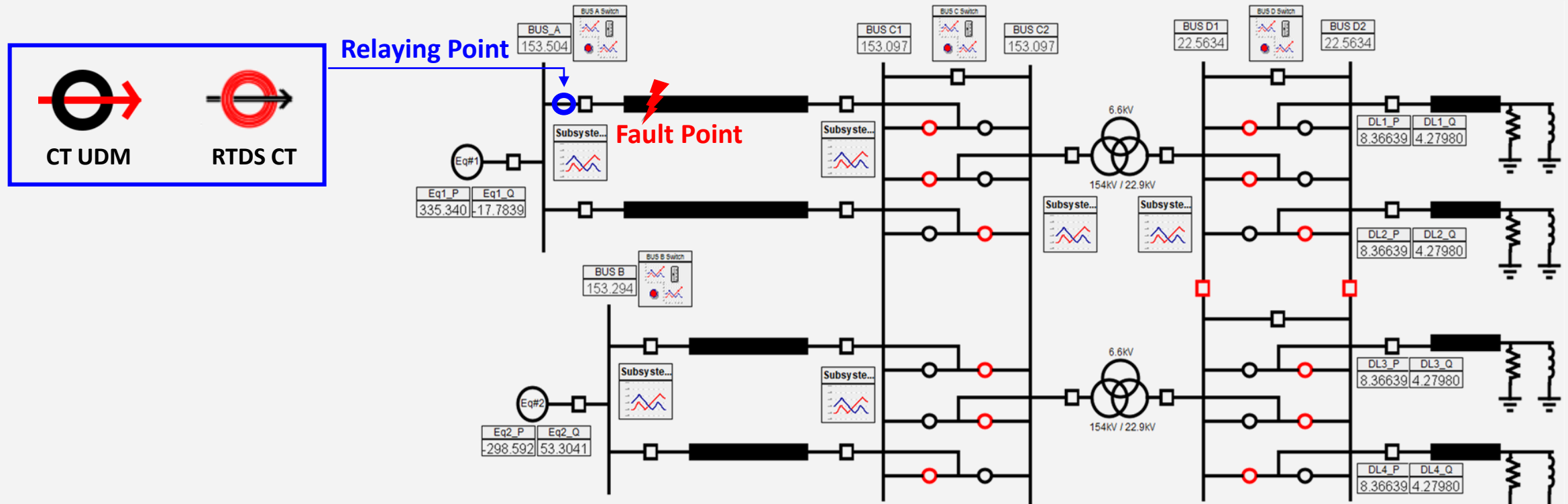

SIMULATION STUDIES

Apply CT UDM to the power system

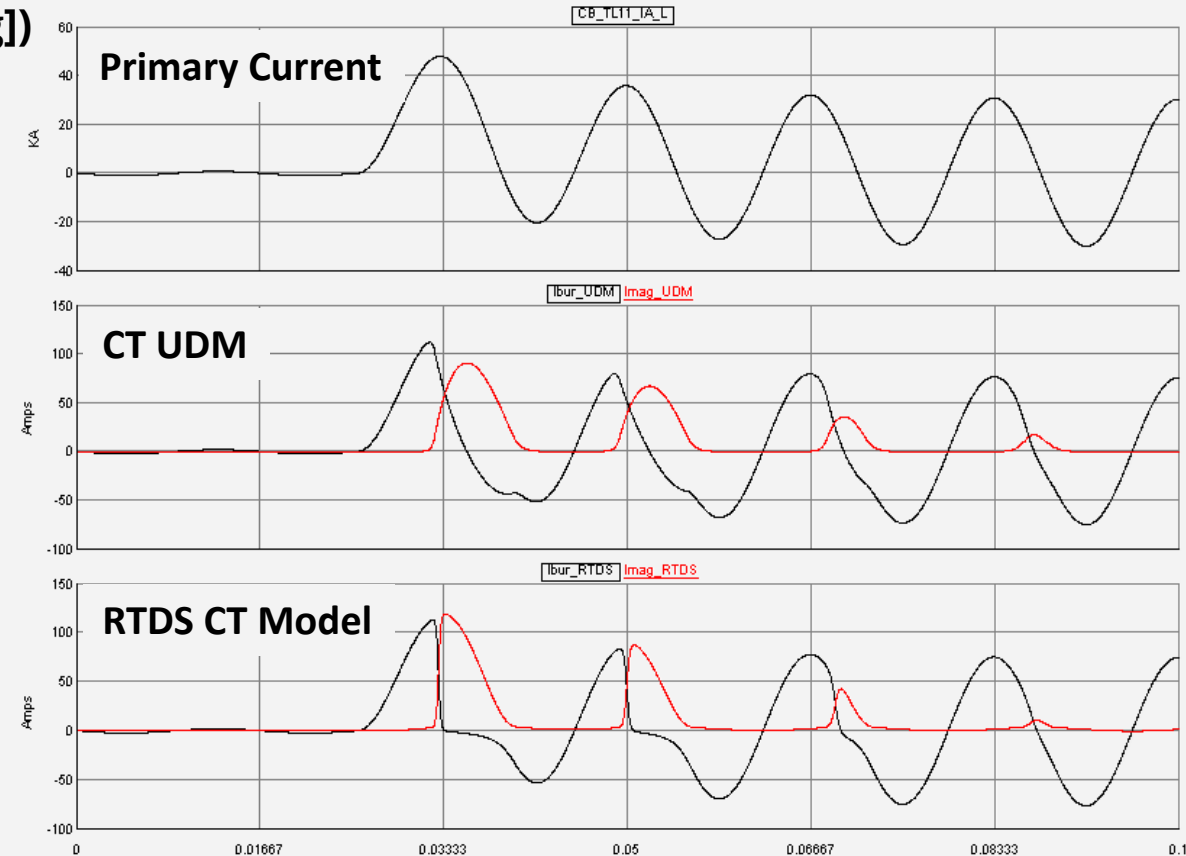
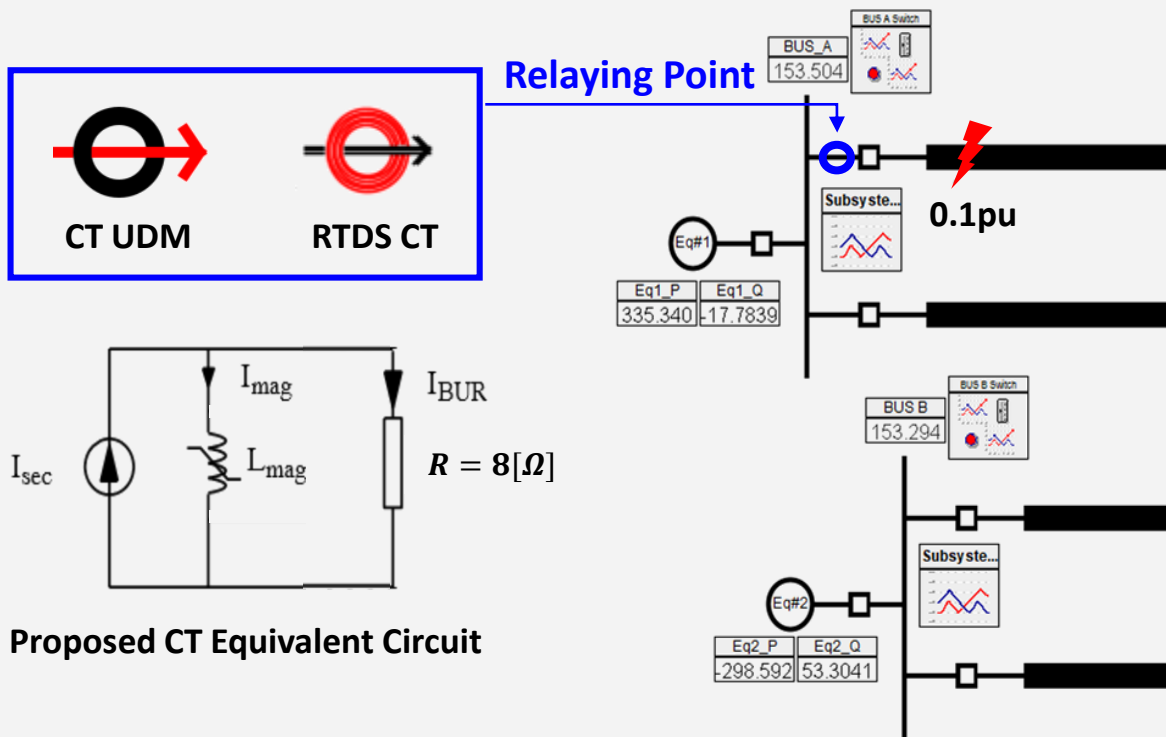
- Single Line to Ground Fault (Fault Angle : 0[deg])
- CT Load $8[\Omega]$ ($R = 8[\Omega]$ pf 1.0)



SIMULATION STUDIES

Apply CT UDM to the power system

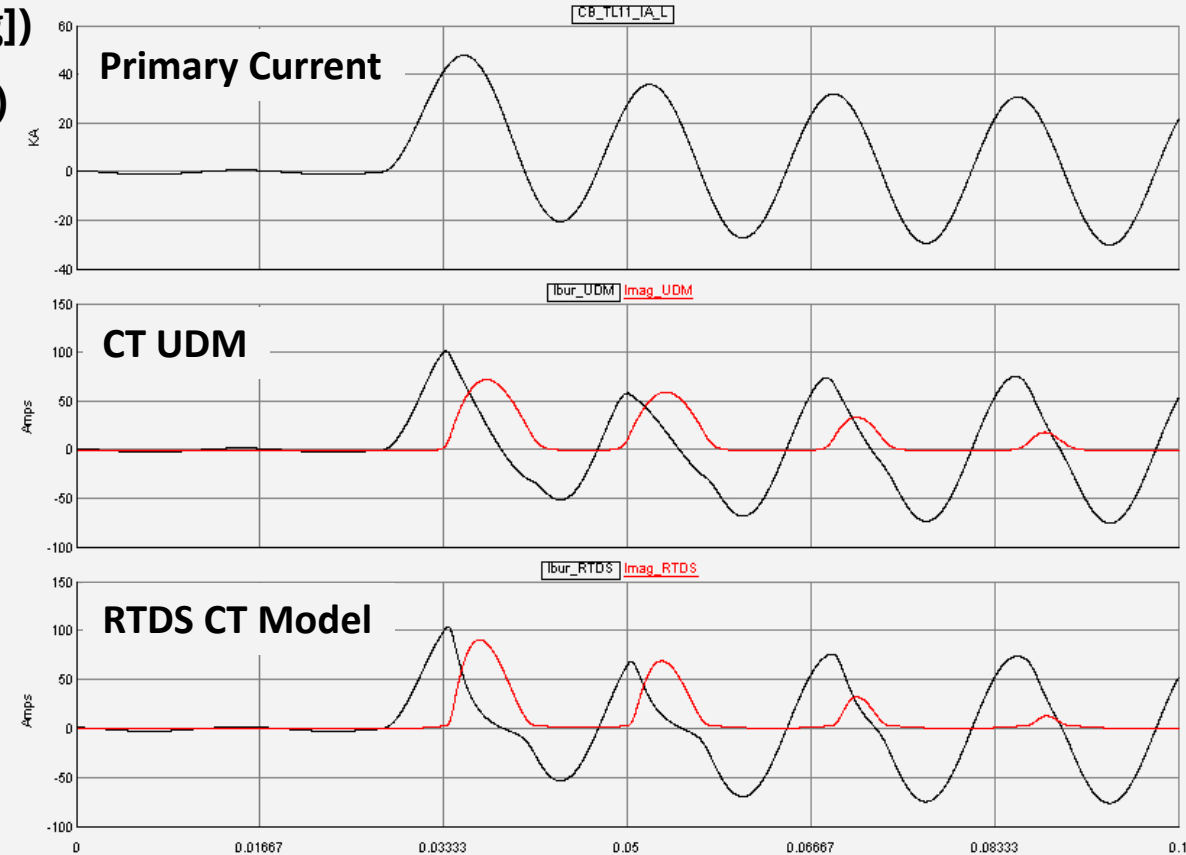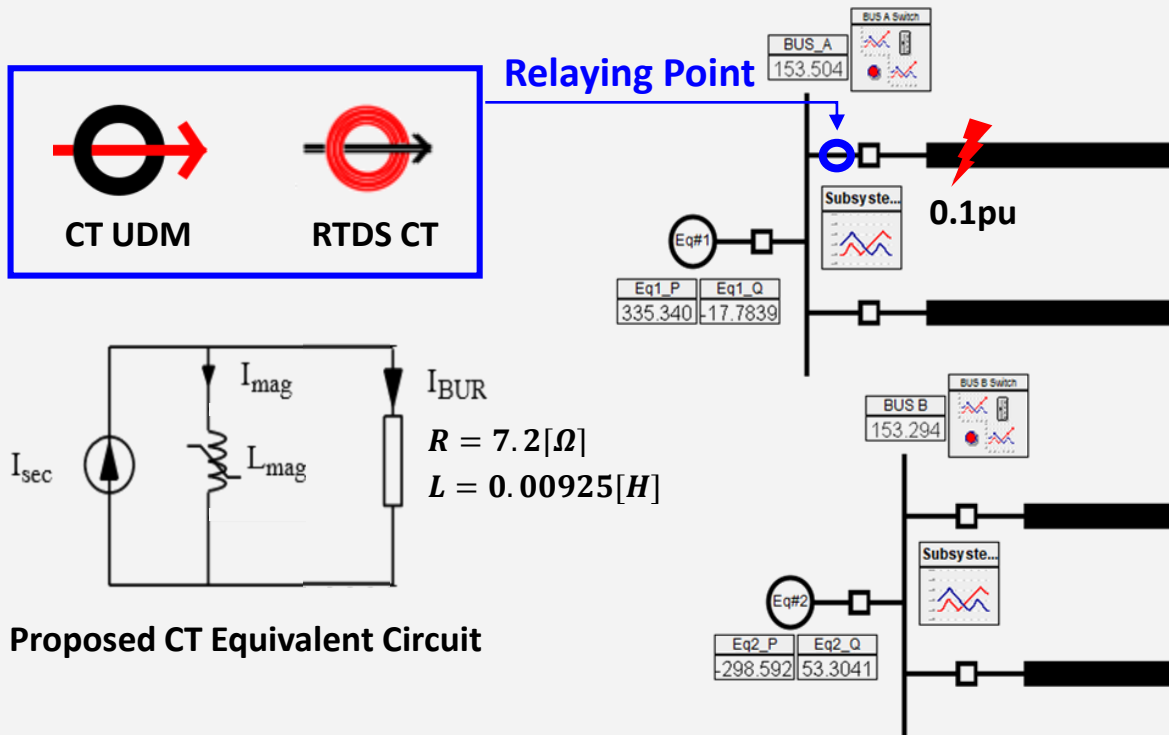- Single Line to Ground Fault (Fault Angle : 0[deg])
- CT Burden 8[Ω] (R = 7.2[Ω], L = 0.00925[H] pf 0.9)



CONCLUSIONS

❖ Summary of the presentation

- When Vrms-Irms data is applied to the RTDS CT model, the curve obtained from its simulation is a bit different from the applied Vrms-Irms data
- CT UDM which accurately reflects input data was developed using computation method of the peak data from rms data and network solution technique(nonlinear element is included)
- Verity the performance of the CT UDM by using open circuit test and apply to the power system



Can be regarded as an effective method to simulate the CT saturation phenomenon

❖ Future Studies

- Consider Core Loss (Hysteresis loss & Eddy current loss)
- Consider residual flux simulation

REFERENCES

- ① L. A. N. Neves, H. W. Dommel, "On Modelling Iron Core Nonlinearities", IEEE Transactions on Power Systems, Volume 8, pp. 417 – 425, May 1993.
- ② H. W. Dommel, "Nonlinear and time-varying elements in digital simulation of electromagnetic transients", IEEE Trans. Power App. Syst., vol. PAS-90, pp. 2561-2567, Nov./Dec. 1971.
- ③ RTDS "POWER SYSTEM COMPONENTS MANUAL"



THANK YOU FOR YOUR ATTENTION