

# DC Transformer Modelling & Simulation in RTDS Simulator

*Xianghua Shi*

*RTDS Technologies Inc.*

*Oct. 18, 2019*



**RTDS**  
Technologies

RTDS.COM

# AGENDA

- **Background**
- **Operation and Control of DC Transformer**
- **DC Transformer Simulation in SUBSTEP**
- **DC Transformer Simulation in GPES**
- **Conclusions & Future Plan**





# Background



RTDS.COM





# DC Transformer

- Power electronic transformer (PET)
- Isolation for input and output sides
- Bidirectional power flow if using fully-controllable switching devices
- High switching frequency → Reducing transformer's cost, volume and weight
- DC Transformer in series/parallel → Large system
 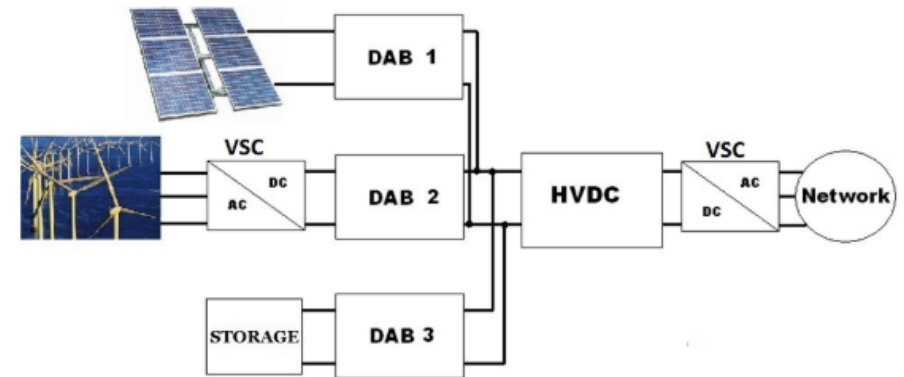
## Applications:


- Automotive
- DC grids
- Renewable energy conversion systems
- Integrating battery energy storage systems
- Medium-voltage or -power systems



# Power Electronics Simulation Capability in RTDS

 
## SubStep Simulation Environment

- Only available on NovaCor hardware platform
- No limit on the number of resistive switching elements\*
- No fictitious losses\*
- Full decomposition allows accurate calculations


 
## GPES Simulation Environment

- A generic PE solver platform on GTFPGA
- Uses powerful parallel processing power of FPGA
- Can model power circuits with arbitrary circuit configurations
- Larger network (128 nodes and 256 branches) and smaller time step (400+ ns), e.g., dc breaker needs 110+ nodes and 200+ switches






# Operation and Control of DC Transformer



# Dual-Active Bridge (DAB) Converter
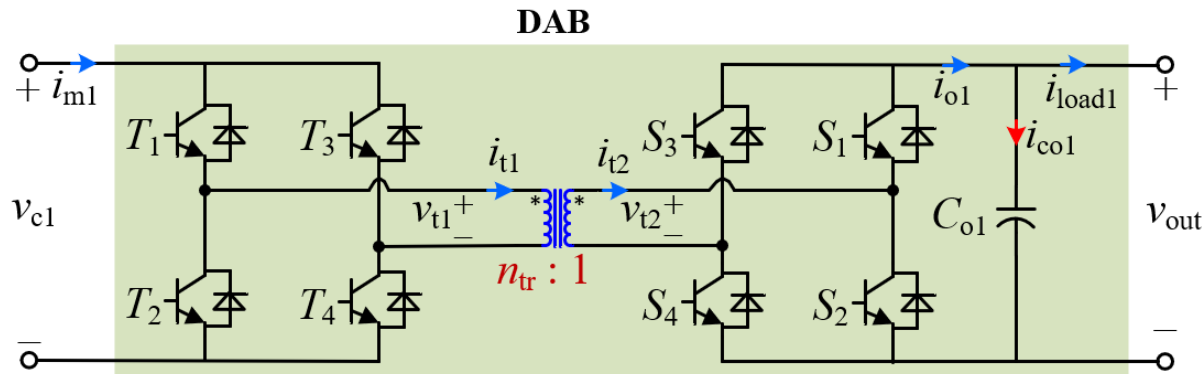
## Operation:

- Considering square-wave operation at both transformer's sides





$$P_{DAB1} = \frac{V_{in} \cdot V_{out} \cdot n_{tr}}{2 \pi \cdot f_{sw} \cdot L_{DAB}} \cdot \varphi \cdot \left(1 - \frac{|\varphi|}{\pi}\right)$$

$0 < \varphi < \pi$ ,  $P_{DAB1} > 0$ : power delivered from  $v_{t1}$  side to  $v_{t2}$  side

$-\pi < \varphi < 0$ ,  $P_{DAB1} < 0$ : power delivered from  $v_{t2}$  side to  $v_{t1}$  side

  → Overall, the power is delivered from leading phase side to lagging phase side.



Phase shift angle:  $\varphi = 2\pi f_{sw} \Delta t$

$\varphi > 0 \rightarrow v_{t1}$  leading  $v_{t2}$

$\varphi < 0 \rightarrow v_{t1}$  lagging  $v_{t2}$

$$I_{m1\_avg} = I_{o1\_avg} / n_{tr}$$

# Leakage Inductance of Transformer

## Design consideration of leakage inductance:

- Considering all the inductance provided by transformer's leakage inductance
- DAB real power < transformer's MVA to avoid overload for transformer
- $V_{in} = k_1 \cdot V_{tr1}$ , and  $V_{out} = k_2 \cdot V_{tr2}$

DAB real power:

$$P_{DAB1} = \frac{V_{in} \cdot V_{out} \cdot n_{tr}}{2 \pi \cdot f_{sw} \cdot L_{lk}} \cdot \varphi \cdot \left(1 - \frac{|\varphi|}{\pi}\right) < S_{tr}$$

TR's turns ratio:

$$\frac{V_{tr1}}{V_{tr2}} = n_{tr}$$

TR's leakage inductance:

$$X_{lk} = 2 \pi \cdot f_{sw} \cdot L_{lk} = \frac{X_{tr} \cdot V_{tr1}^2}{S_{tr}}$$

Input and output voltage:

$$V_{in} = k_1 \cdot V_{tr1} \quad V_{out} = k_2 \cdot V_{tr2}$$

$X_{tr}$ : transformer's leakage inductance in p.u.

$$\frac{V_{in} \cdot V_{out}}{V_{tr2}^2} \cdot \frac{1}{X_{lk} \cdot n_{tr}} \cdot \varphi \cdot \left(1 - \frac{|\varphi|}{\pi}\right) < 1$$

- Typically, in rated operation,  $V_{in} = V_{tr1}$ , and  $V_{out} = V_{tr2}$ , i.e.,  $k_1 = 1$ ,  $k_2 = 1$ ,  $n_{tr} = V_{in}/V_{out}$


$$X_{tr} > \varphi \cdot \left(1 - \frac{|\varphi|}{\pi}\right)$$

If  $\varphi_{sel} := 25 \text{ deg}$        $\varphi_{sel} \cdot \left(1 - \frac{|\varphi_{sel}|}{\pi}\right) = 0.376$



$$X_{tr} > 0.376 \text{ pu}$$


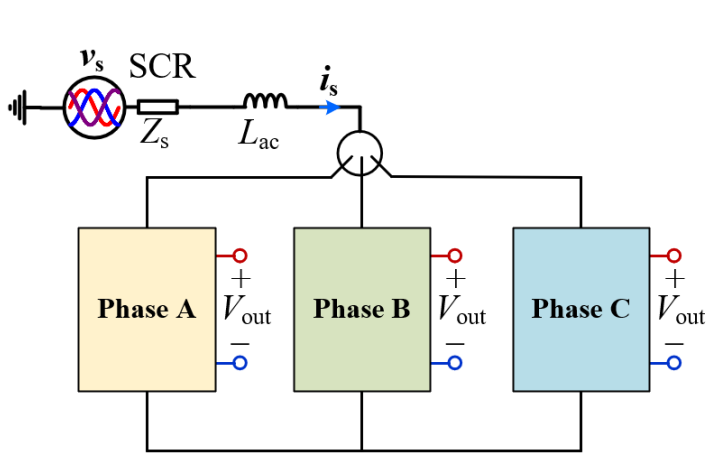
# Application: AC Grid → MMC → DAB → Load




Full-bridge + DAB

 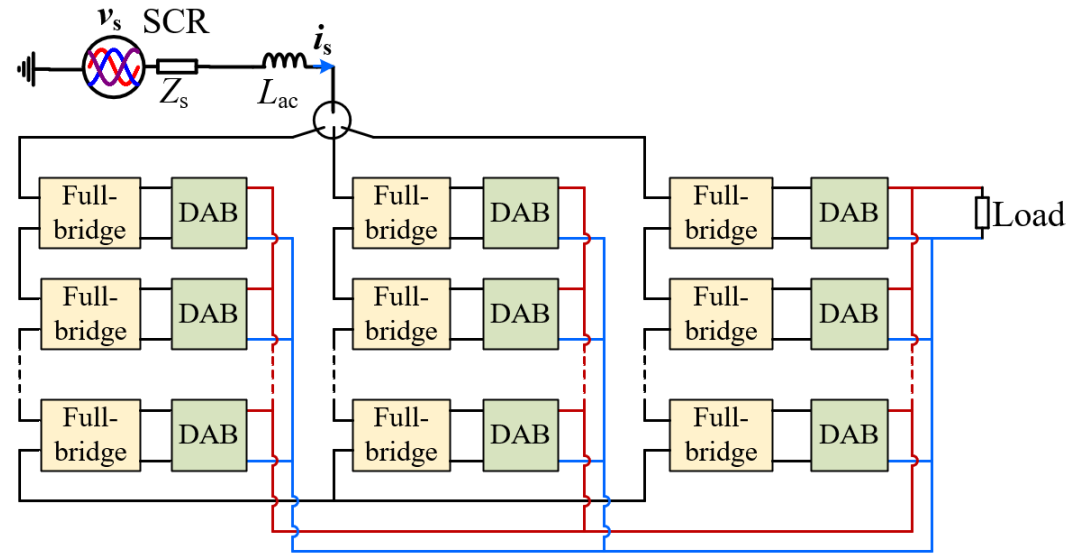

## H-bridge AC-DC stage:

- Similar to control requirements of conventional MMC
  - Real power or capacitor voltage controls
  - Capacitor **voltage balancing** control

## DAB

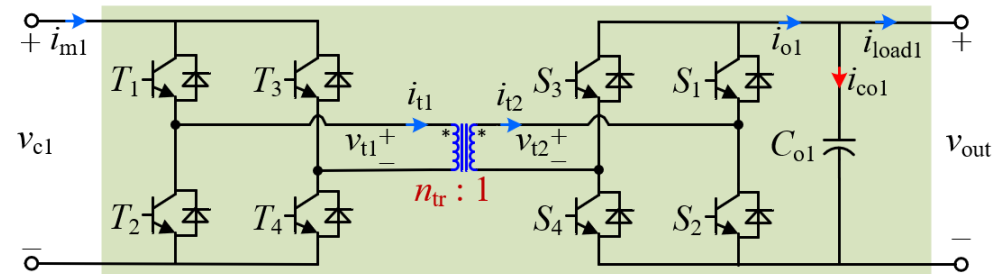




## DAB power/voltage control:

- It adjusts phase shift between  $v_{t1}$  and  $v_{t2}$

# Capacitor Voltage Balancing Control
 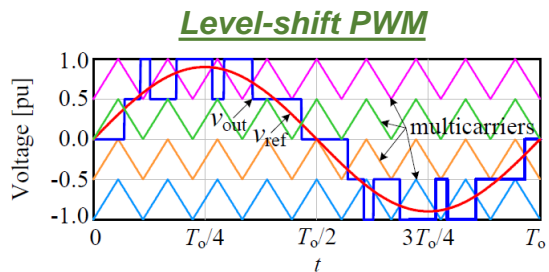 
## Method I:



- Switching frequency for Switches is varying, maximum at equivalent PWM frequency
- No needs of PI parameters



- NLC: mainly used for a large number of submodules
- Multicarrier-based PWM: can be used for either a large or small number of submodules

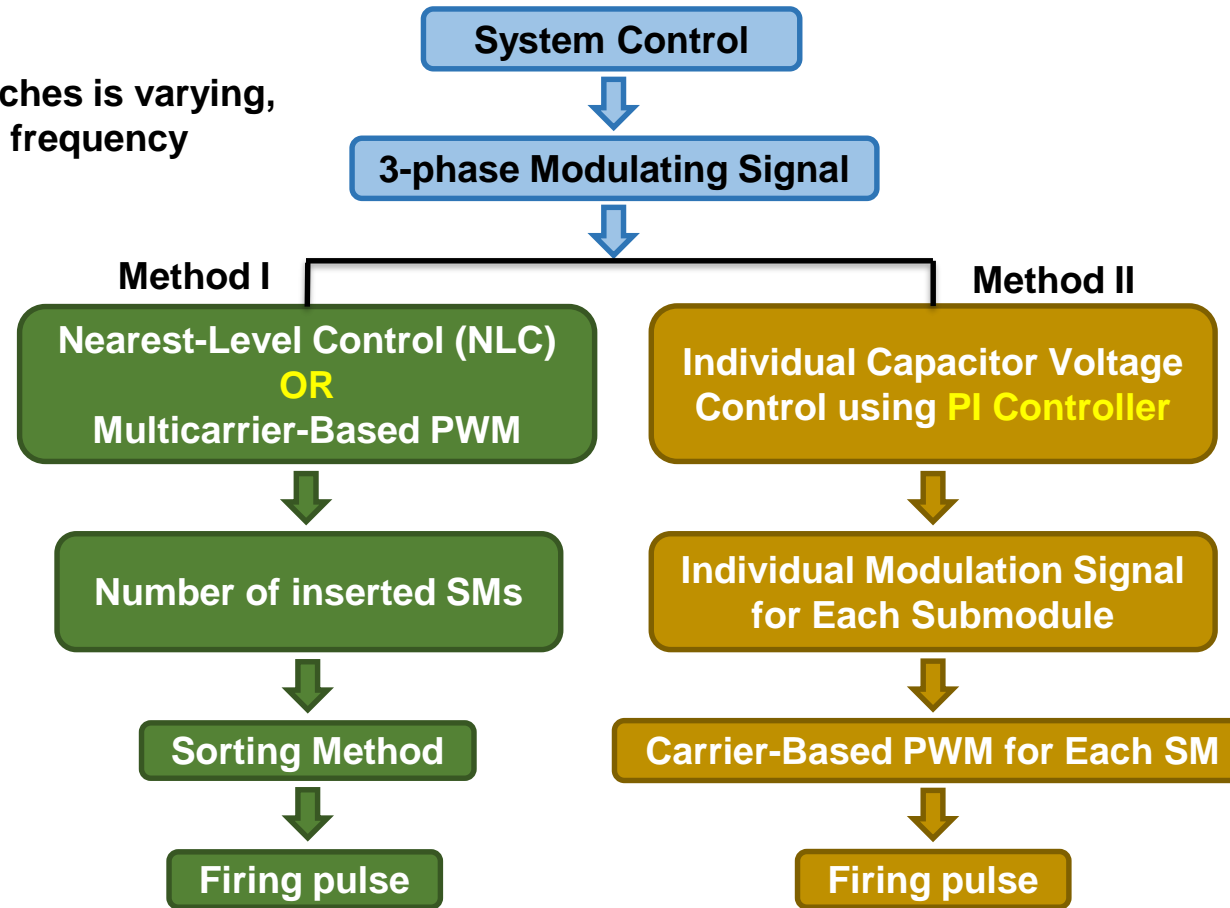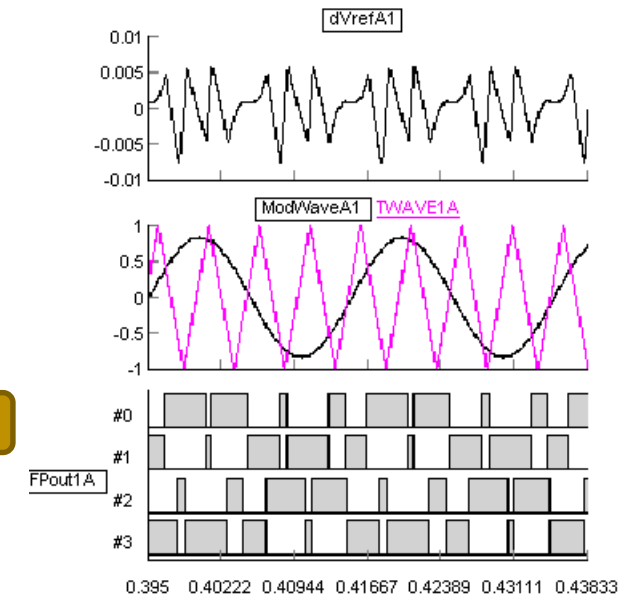
## Method II:

- Switching frequency for Switches is fixed at carrier frequency
- It needs to design PI parameters


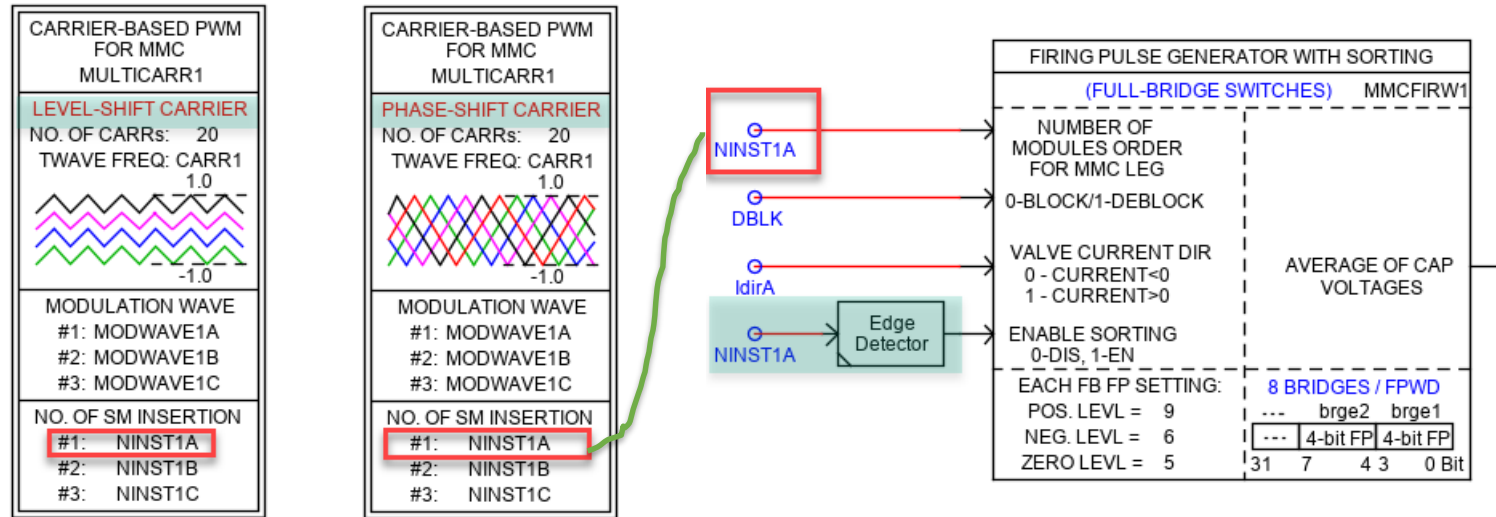
# NEW Control Component Development for Capacitor Voltage Balancing – (SORTING METHOD)


- **Multicarrier-based PWM**
- **Firing Pulse Generator with Sorting**
- It supports up to 32 submodules in series
- It supports Level- or Phase-shift PWM
- Firing pulse arrangement in a word supports **customer-specified**
- It supports firing pulses for **Half- or Full-bridge** submodule switches and **CHAINV5** MMC Model



*For Half-bridge with switches*

Name	Description	Value	Unit	Min	Max
poslevlhb	FP Value for Positive Voltage Level Output:	1		0	3
zerolevlhb	FP Value for Zero Voltage Level Output:	2		0	3


Level	T2	T1	Value
Pso	0	1	1
Zero	1	0	2

 

*For Full-bridge with switches*

Name	Description	Value	Unit	Min	Max
poslevlfb	FP Value for Positive Voltage Level Output:	9		0	15
neglevlfb	FP Value for Negative Voltage Level Output:	6		0	15
zerolevlfb	FP Value for Zero Voltage Level Output:	5		0	15


Level	T4	T3	T2	T1	Value
Pso	1	0	0	1	9
Neg	0	1	1	0	6
Zero	0	1	0	1	5
	1	0	1	0	10

 

# NEW Control Component Development for Capacitor Voltage Balancing – (PI CONTROL METHOD)

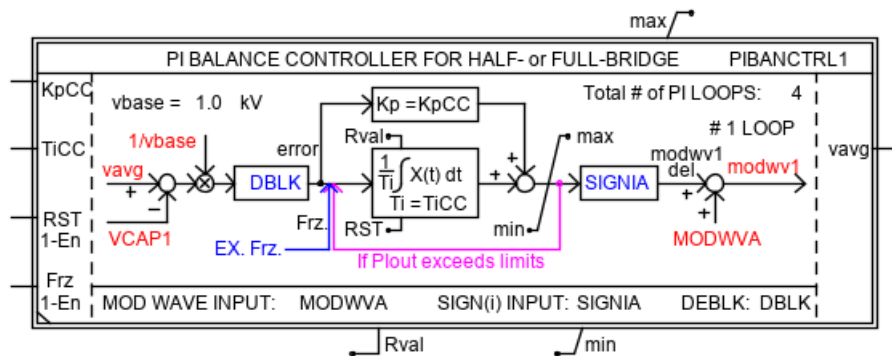
## ➤ Multiple PI Controller

- It supports up to 32 PI control loops
- PI controller configuration supports RESET, FROZEN, and LIMITS
- It outputs individual modulation signal for each submodule


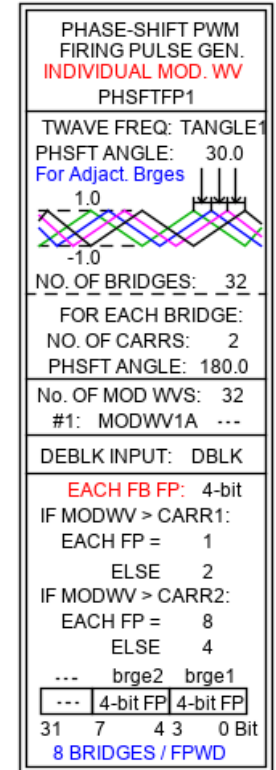
## ➤ Flexible Phase-Shift PWM Firing Pulse Generator

- It supports various PWM pattern:
  - ONE modulation signal with multiple carriers
  - Individual modulation signal with each carrier
  - One or Two carriers for each modulation signal
- Firing pulse arrangement in a word supports **customer-specified**
- It supports firing pulses for **Half- or Full-bridge** submodule switches and **CHAINV5** MMC Model



Name	Description	Value	Unit	Min	Max
Name	PHASE-SHIFT PWM FP GENERATOR NAME:	PHSFTFP1v2			
brgetype	Firing Pulse to Drive Half or Full Bridge?	Full		0	1
numbrge	No. of Bridges:	32		0	32
modeltype	Bridge Model: Separate Switches or CHAINV5?	Separate Switches		0	1
modwvtype	No. of Modulation Waves to All Bridges:	One		0	1
numcarr1	No. of Carriers for Each Bridge:	One		1	2
phsft1	– IF 2 Carriers, Phase Shift (>0 lead, <0 lag):	Individual	Degrees	-360.0	360.0
ndebk	Overall De-block Signal (0-blk, 1-deblk) Name:	DBLK			





# DC Transformer Simulation in SubStep






# System Parameters

Parameter	AC-DC Stage	DC Transformer (DAB)
# of modules	6 Full-bridge SMs in series	6 DABs in parallel
AC grid	10 kV (LL, rms), 50 Hz, $Z_s = 3.5 \Omega + j\omega_0 * 0.1 \text{ mH}$	N/A
DC output	1.5 kV, 4700 uF / Full-bridge	1.5kV, 50 uF / DAB
PWM modulation	Unipolar dual-frequency SPWM	Phase-shift PWM with duty = 0.5 (square-wave)
Carrier frequency	200 Hz	1.0 kHz
Transformer	N/A	1.5 kV:1.5 KV, 0.125 MW, 1.0 kHz, 36.7% leakage
Cap Voltage Balancing	<b>PI control balancing method</b>	N/A
Real power	2.25 MW	

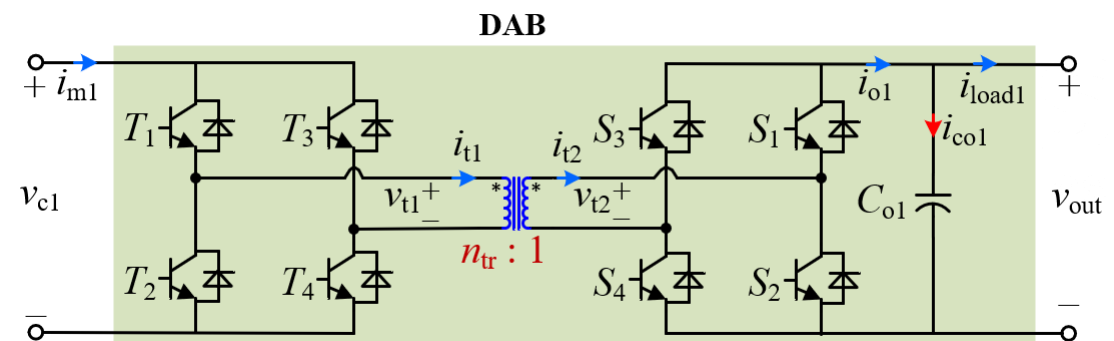
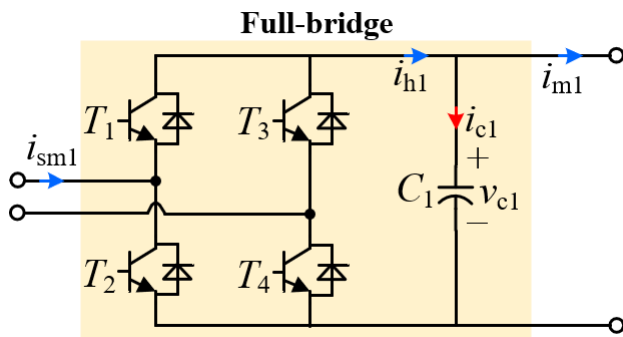


# System Control

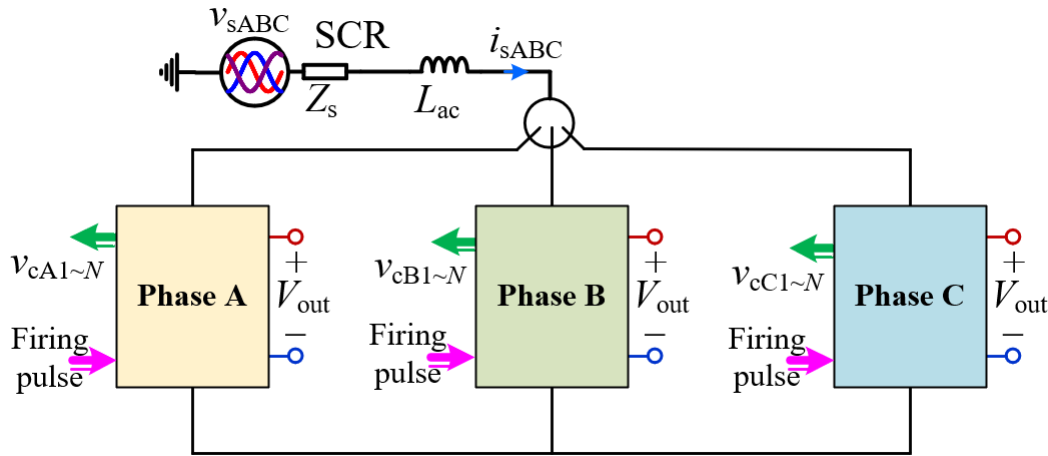

  
## DABs:

- **Output voltage control:** generate Phase Shift for two sides of one DAB
- **Parallel operation:** use phase-shift PWM to increase harmonic frequency
- **Square-wave operation:** duty = 0.5





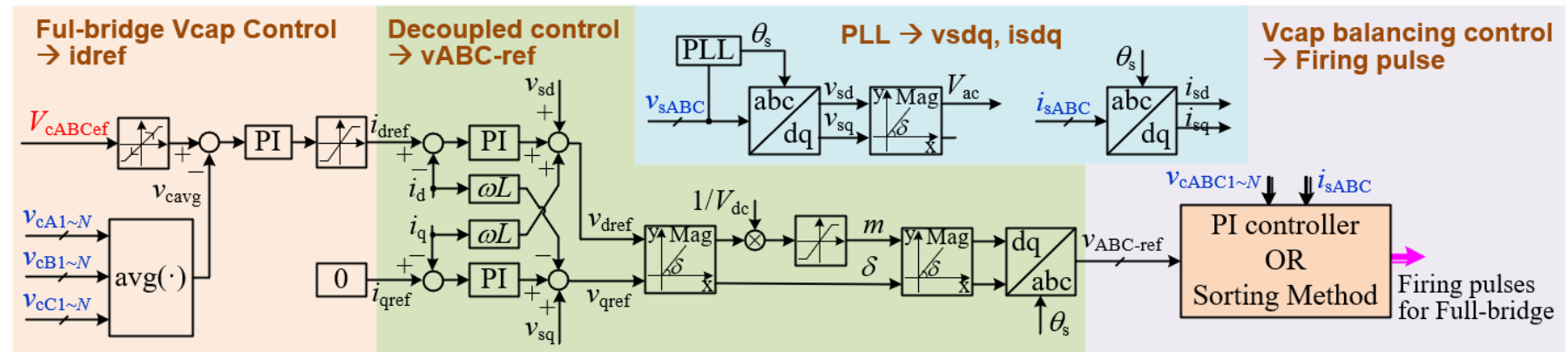
## AC-DC stage:

- **Vcap control + current decoupled control:** generate 3-phase references
- **Vap balancing**
- **PWM method:** Unipolar dual-frequency SPWM



 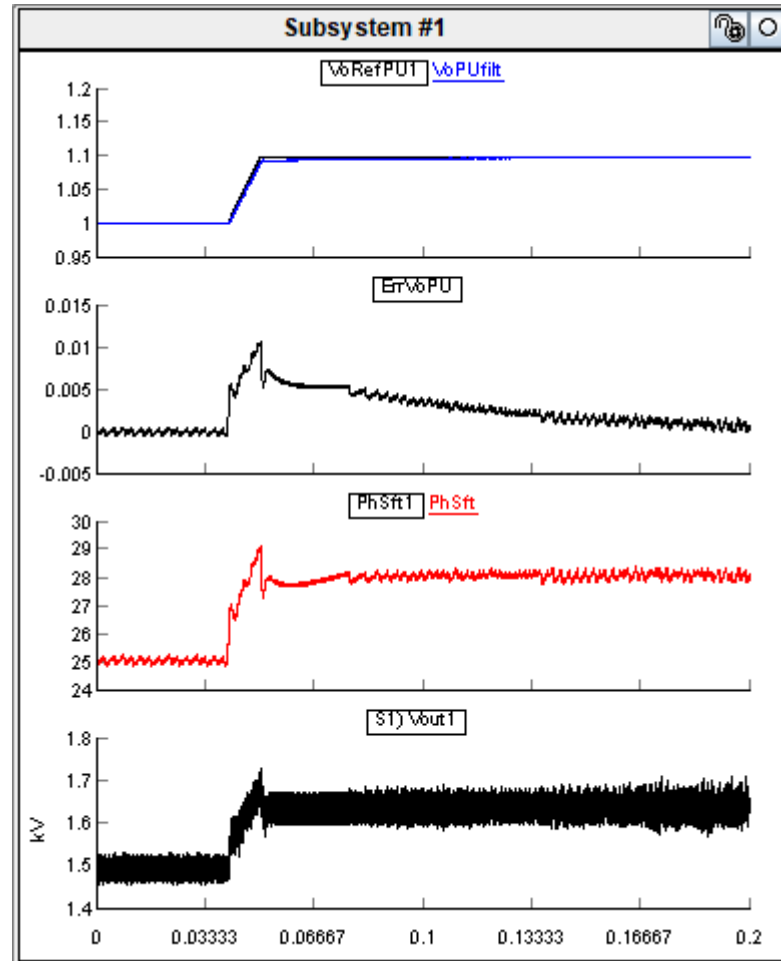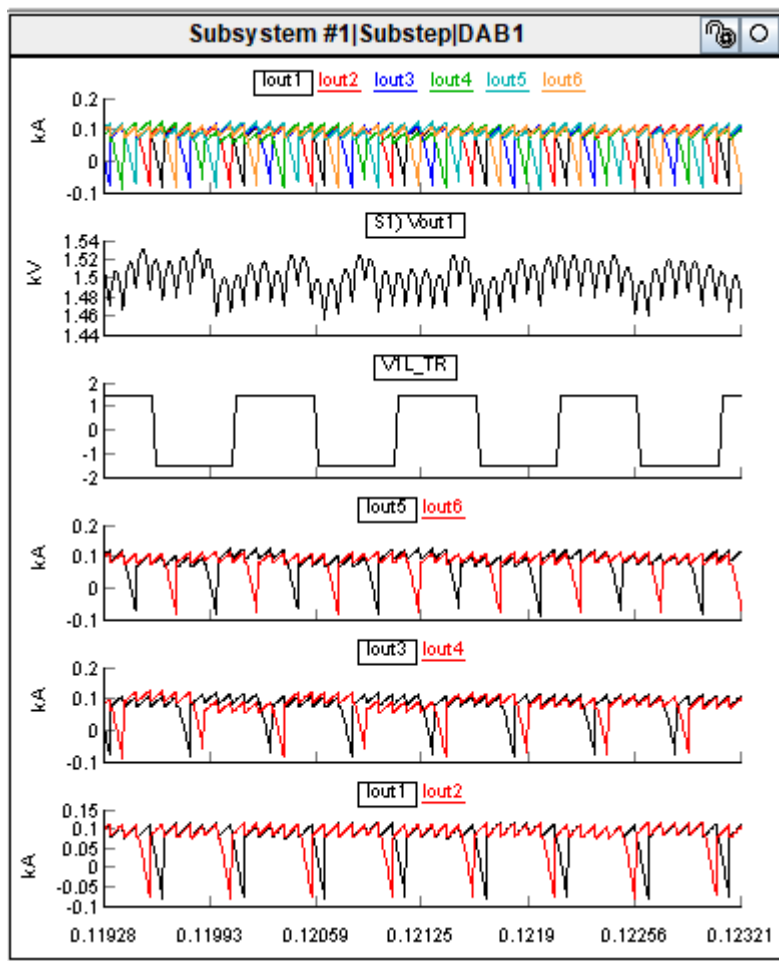
# Phase-Shift PWM for DABs in Parallel Operation



The paralleled output voltage and current harmonic frequency is significantly increased, which potentially permits the decrease of output capacitance.

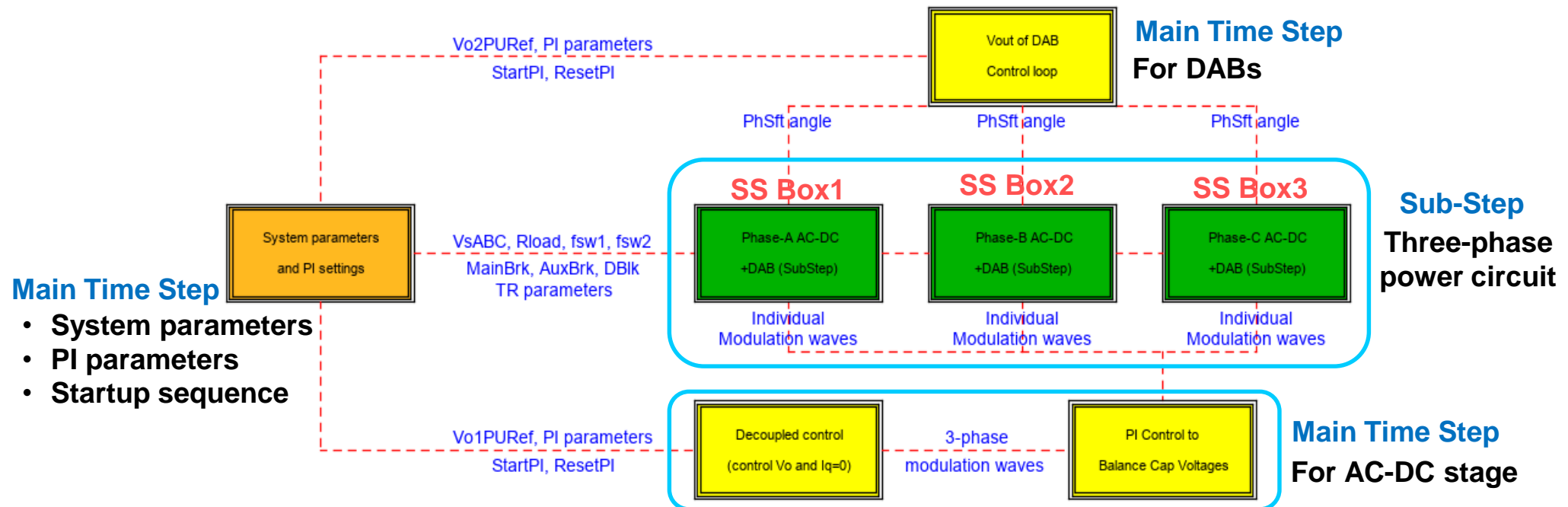
# SUBSTEP Simulation (AC-DC + DAB)

- Resistive switching model
- Main time step: 45 us
- Sub-timestep: 45 us/5 = 9 us
- # of modules per phase:  $N = 6$  (18 H-bridges + 6 Transformers)/phase
- Substep box: 112 models, 53 nodes



- System parameters
- PI parameters
- Startup sequence



# Circuit in One SubStep Box and Firing

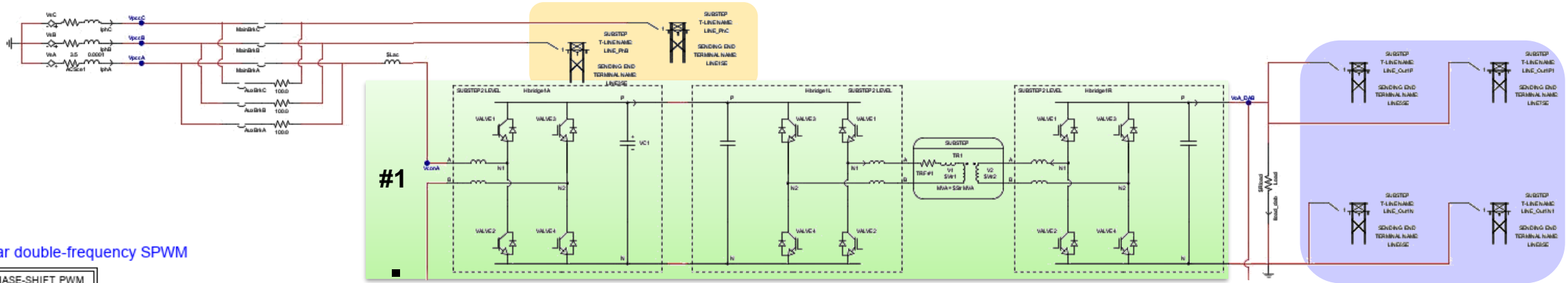


Unipolar double-frequency SPWM

PHASE-SHIFT PWM FIRING PULSE GEN. INDIVIDUAL MOD. WV PHSFTFP1	
TWAVE ANGLE:ANGLE PHSFT ANGLE: -30.0 For Adjact. Brges	
NO. OF BRIDGES: 6	
FOR EACH BRIDGE: NO. OF CARRS: 2 PHSFT ANGLE: 180.0	
No. OF MOD WVS: 6 #1: ModWaveA1 ...	
DEBLK INPUT: DBik	
EACH FB FP: 4-bit IF MODWV > CARR1: EACH FP = 1 ELSE 2 IF MODWV > CARR2: EACH FP = 8 ELSE 4 ... brge2 brge1	
... 4-bit FP 4-bit FP	
31 7 43 0 Bit 8 BRIDGES / FPWD	

Firing pulse generator for AC-DC stage

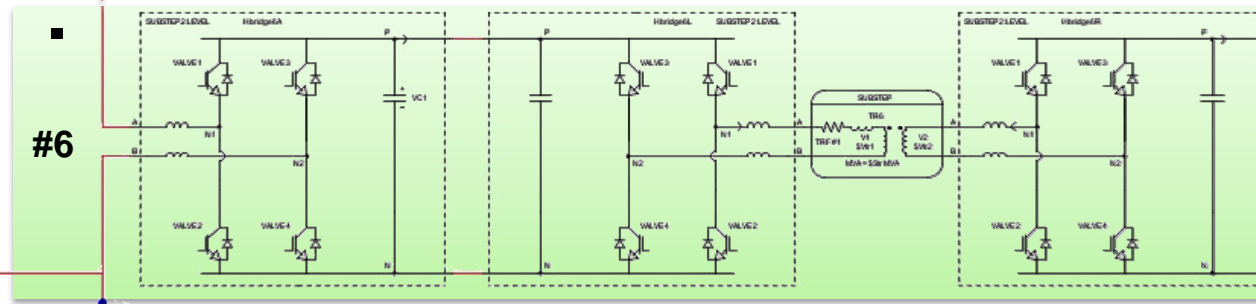 

Firing pulse generator for DAB stage

 


Phase-shift PWM for DABs

PHASE-SHIFT PWM FIRING PULSE GEN. ONE MOD. WAVE PHSFTFP2	
TWAVE ANGLE: AngL1A PHSFT ANGLE: -30.0 For Adjact. Brges	
NO. OF BRIDGES: 6	
FOR EACH BRIDGE: NO. OF CARRS: 1	
No. OF MOD WVS: 1 #1: Duty	
DEBLK INPUT: DBik	
EACH FB FP: 4-bit IF MODWV > CARR1: EACH FP = 9 ELSE 6	
... brge2 brge1	
... 4-bit FP 4-bit FP	
31 7 43 0 Bit 8 BRIDGES / FPWD	


PHASE-SHIFT PWM FIRING PULSE GEN. ONE MOD. WAVE PHSFTFP3	
TWAVE ANGLE: AngR1A PHSFT ANGLE: -30.0 For Adjact. Brges	
NO. OF BRIDGES: 6	
FOR EACH BRIDGE: NO. OF CARRS: 1	
No. OF MOD WVS: 1 #1: Duty	
DEBLK INPUT: DBik	
EACH FB FP: 4-bit IF MODWV > CARR1: EACH FP = 9 ELSE 6	
... brge2 brge1	
... 4-bit FP 4-bit FP	
31 7 43 0 Bit 8 BRIDGES / FPWD	


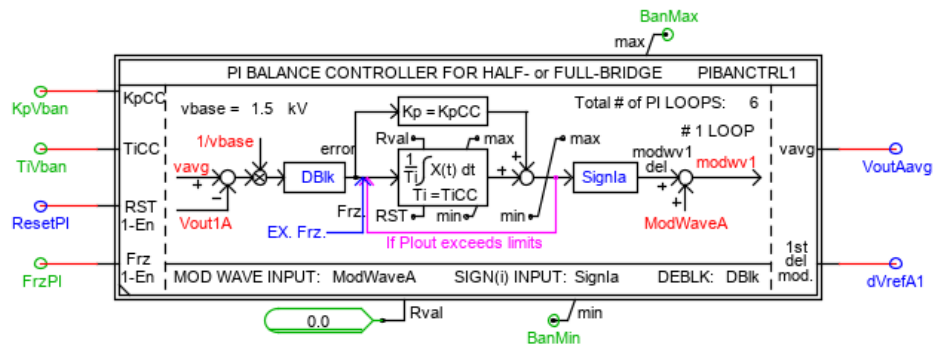
# Phase-A Capacitor Voltage Balancing PI Control Implementation



Using newly developed control component

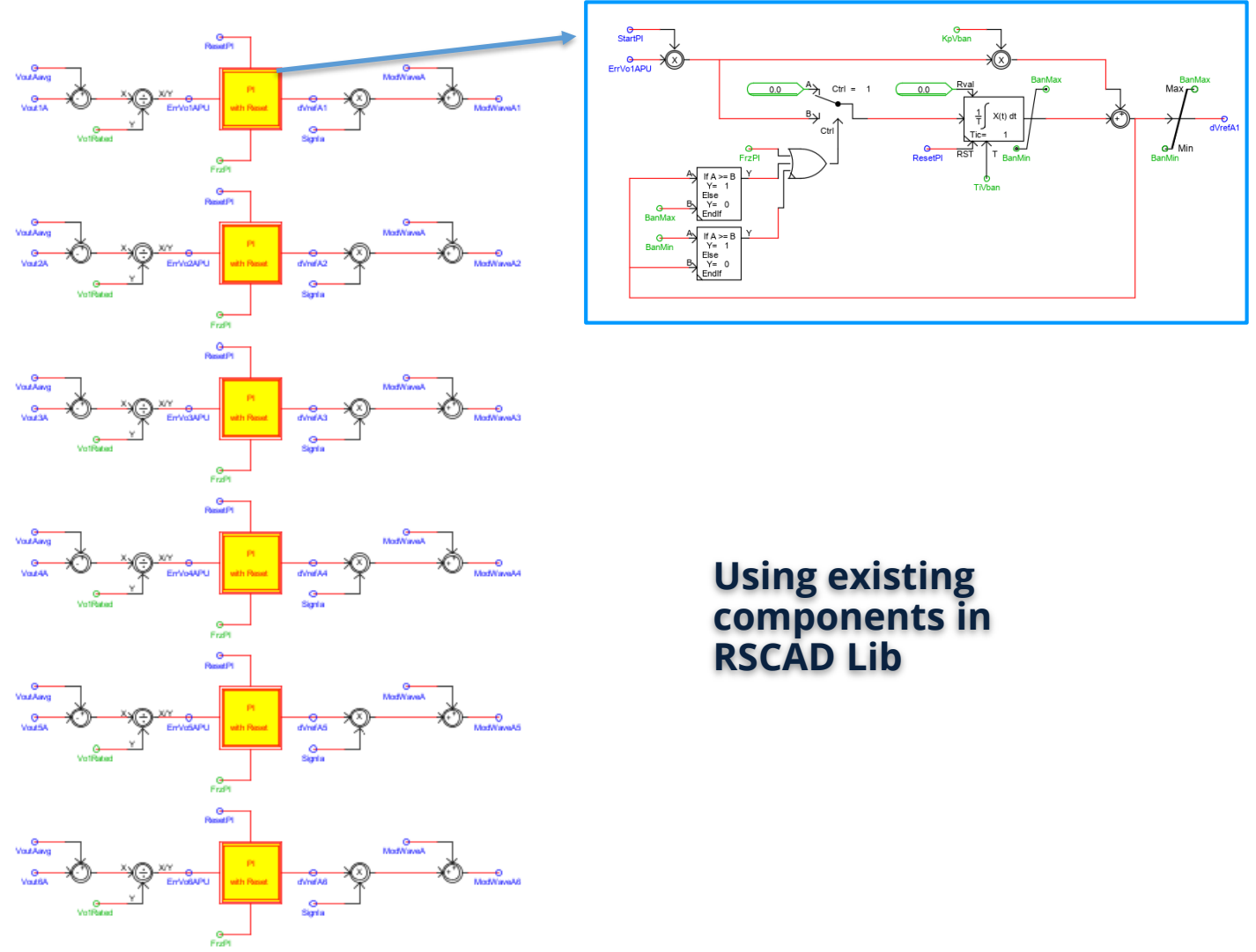

Using existing components in RSCAD Lib






# Phase-Shift PWM Firing Pulse Generation

For 6 modules/phase




For AC-DC stage

For DAB stage

Using existing components in RSCAD Lib

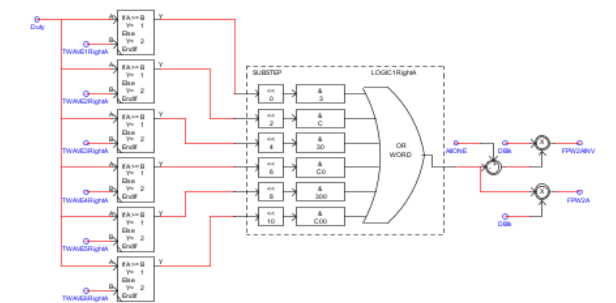   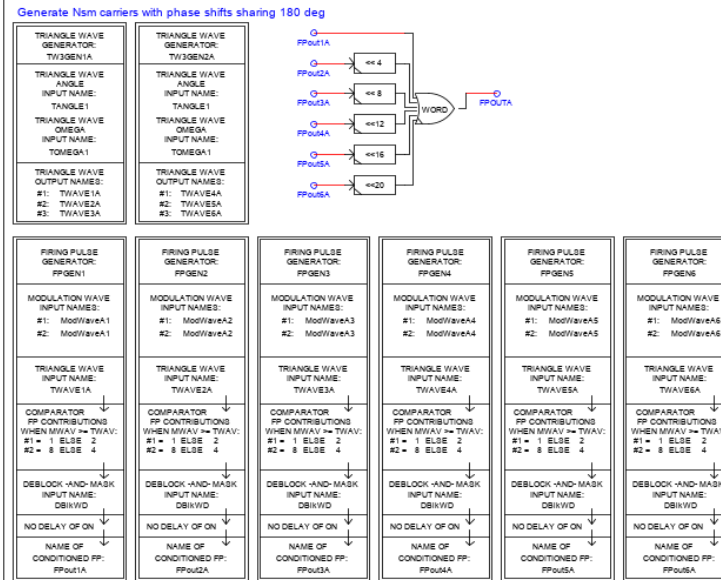


Using newly developed component

   


# SUBSTEP Simulation Results


Blocking → Deblocking

 

AC-DC stage operating waveform

 


AC-DC stage  $V_{cap}$  control loop

 


DAB output voltage control loop
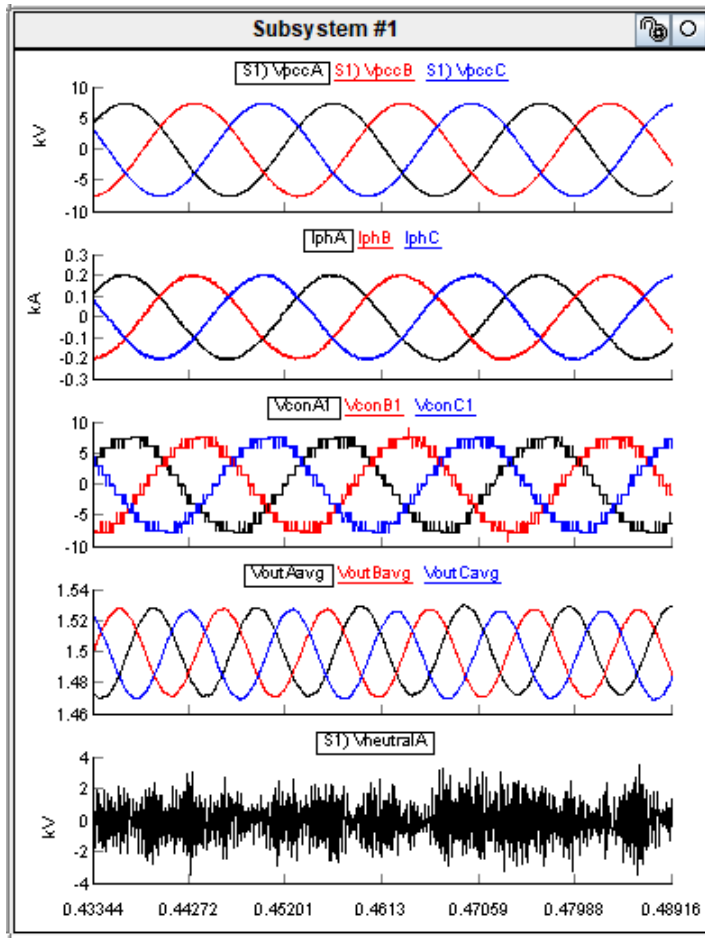
# SUBSTEP Simulation Results


Steady-state operation:  $V_{out} = 1.0 \text{ pu} \rightarrow P_o = 2.25 \text{ MW}$




**AC-DC stage operating waveform**

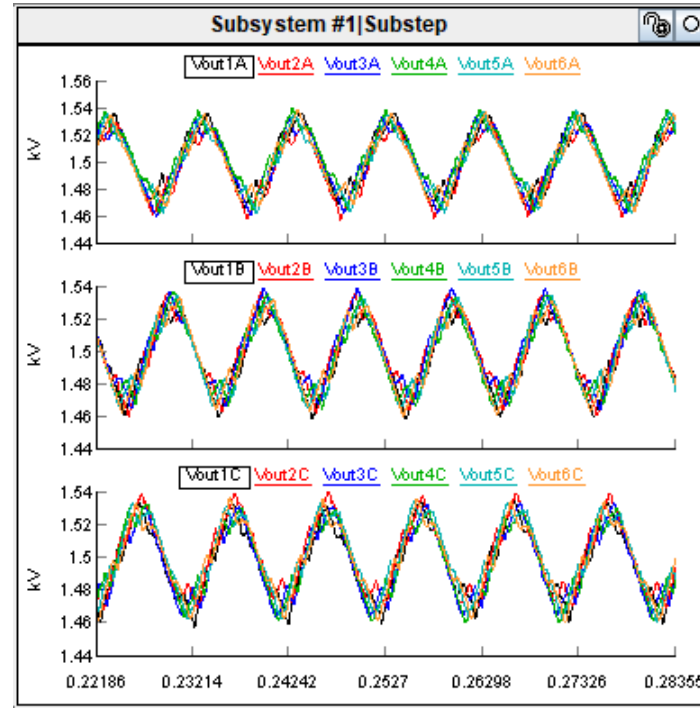

**Cap voltages in AC-DC stage**

 


**DAB output waveforms**

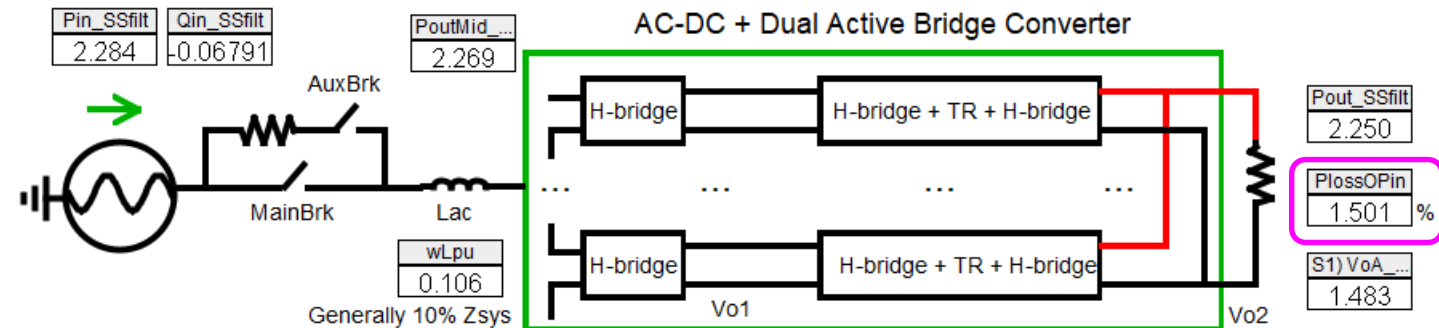

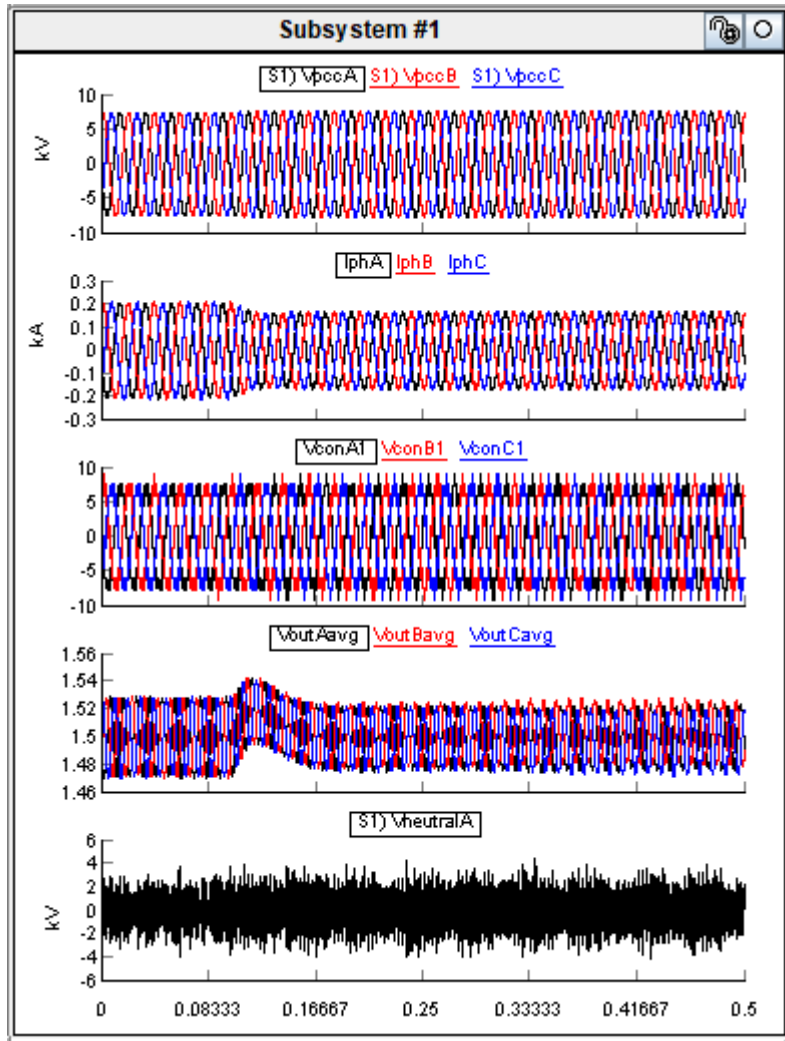
# SUBSTEP Simulation Results


*Dynamic operation:  $V_{out} = 1.0 \text{ pu} \rightarrow 0.9 \text{ pu}$*



**AC-DC stage operating waveform**

 

**AC-DC stage  $V_{cap}$  control loop**

 

**DAB output voltage control loop**






# DC Transformer Simulation in GPES




RTDS.COM
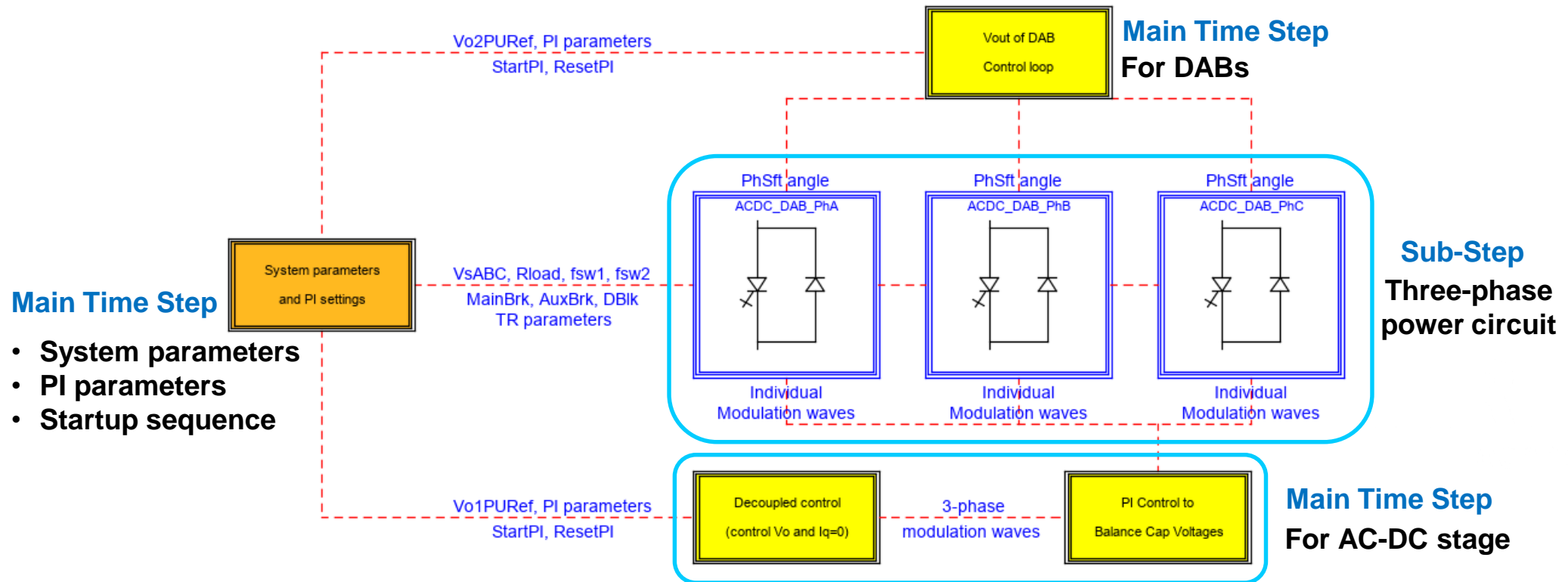
# GPES Simulation in Small-dt Box (AC-DC + DAB)


- Main time step: 45 us
- Small timestep: 2.8125 us
- GPE timestep: 0.9375 us (3 sub-small timesteps)
- # of modules per phase:  $N = 6$  (18 H-bridges + 6 Transformers)/phase
- GPES box: 102 branches, and 47 nodes



# Circuit in One Small-dt Box

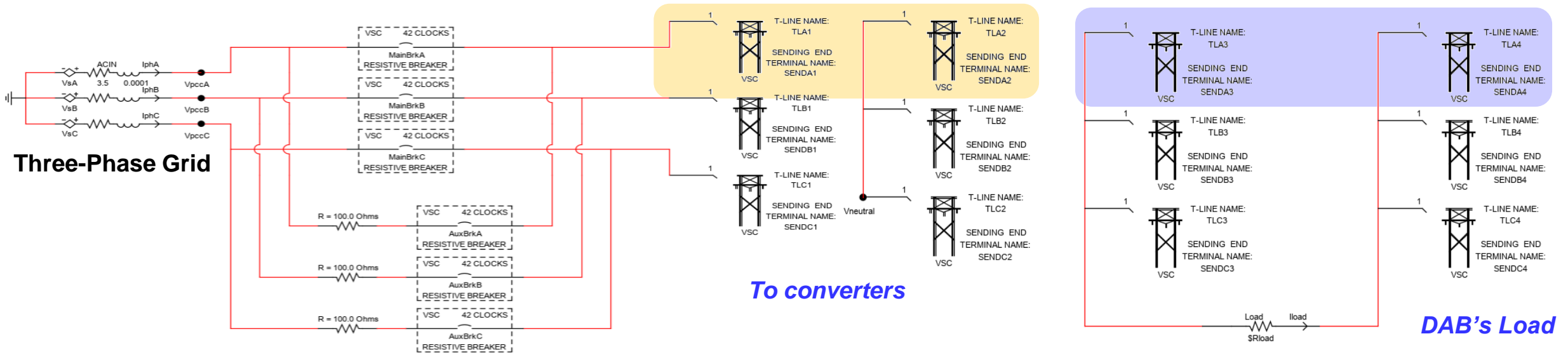


## Phase A (AC-DC + DAB Converters)

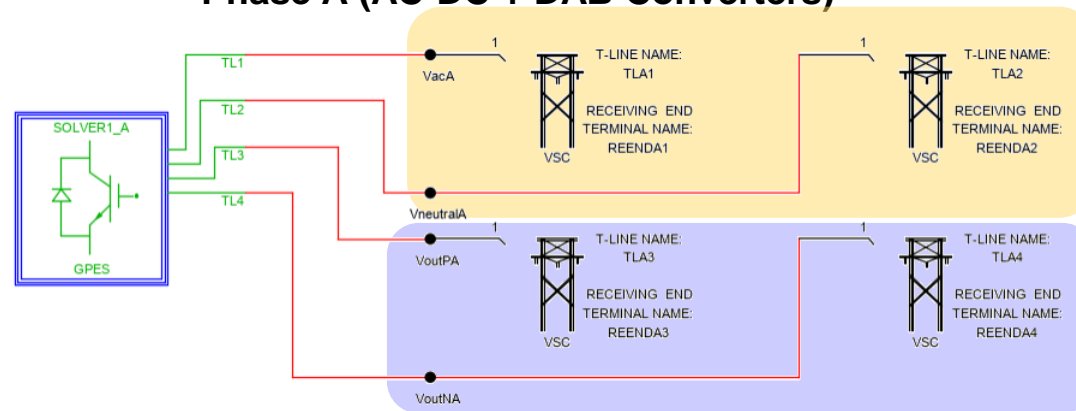


# GPES Simulation Results


Blocking → Deblocking

 

AC-DC stage operating waveform

 


AC-DC stage Vcap control loop

 


DAB output voltage control loop

# GPES Simulation Results

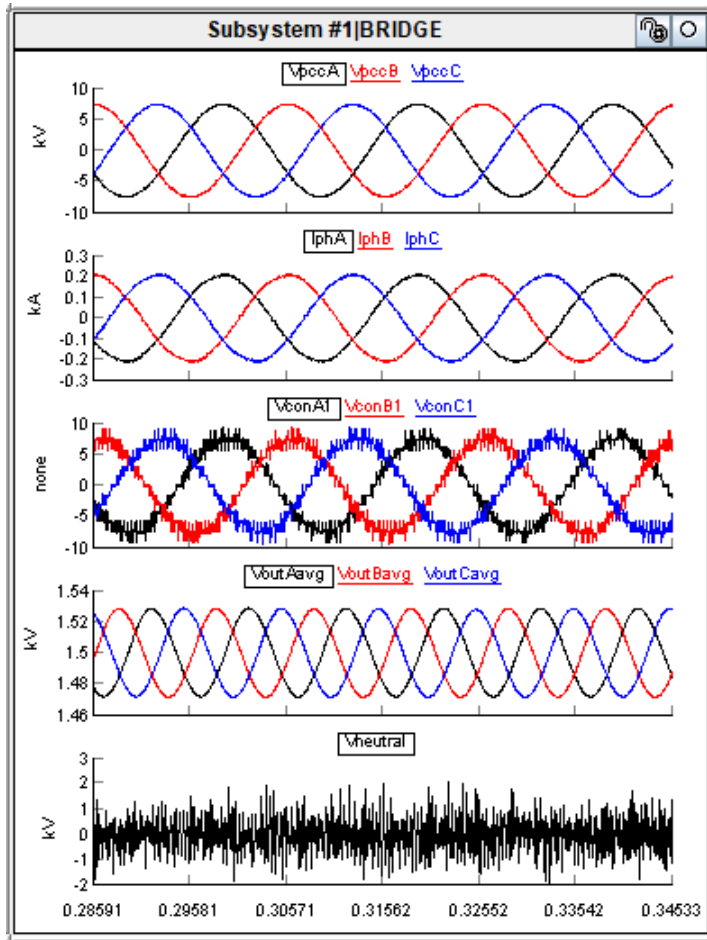
**Steady-state operation:  $V_{out} = 1.0 \text{ pu} \rightarrow P_o = 2.25 \text{ MW}$**



**AC-DC stage operating waveform**

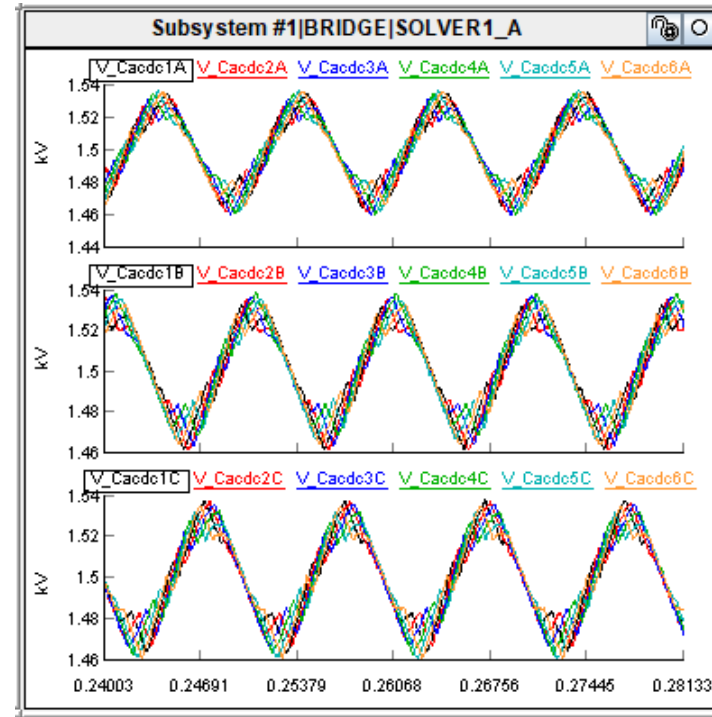


**Cap voltages in AC-DC stage**

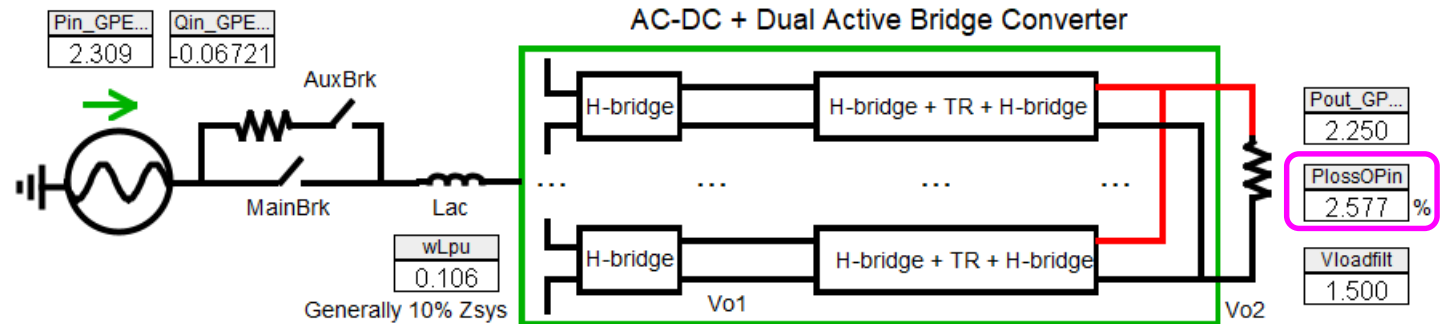



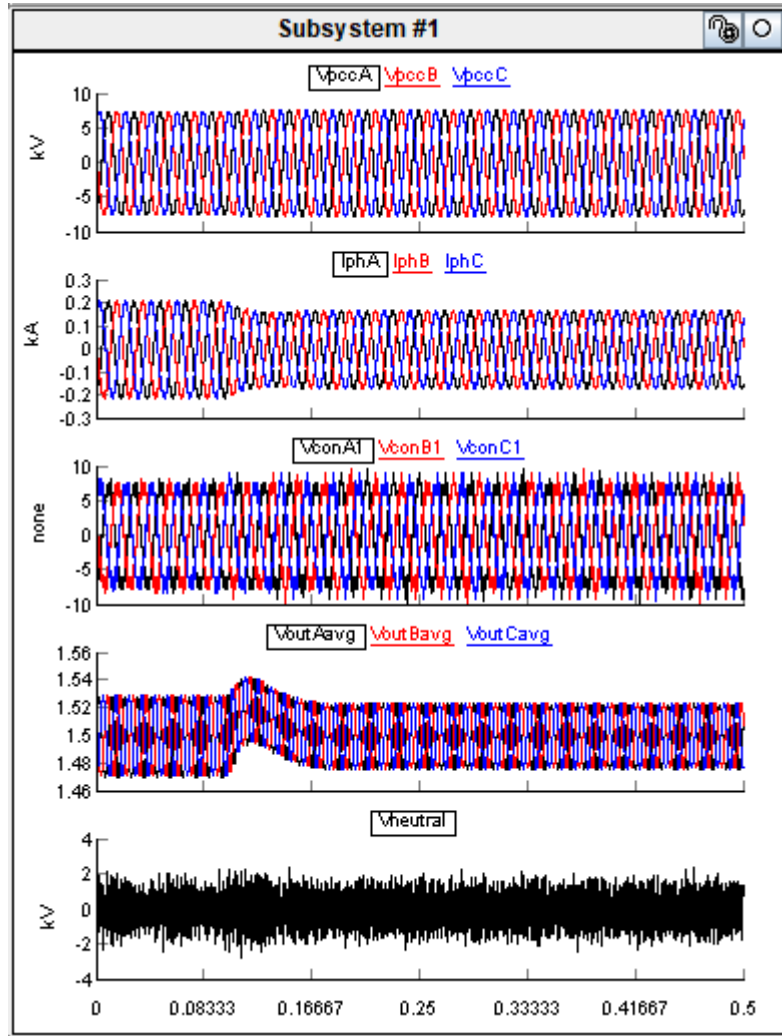
# GPES Simulation Results


*Dynamic operation:  $V_{out} = 1.0 \text{ pu} \rightarrow 0.9 \text{ pu}$*



**AC-DC stage operating waveform**

 

**AC-DC stage  $V_{cap}$  control loop**

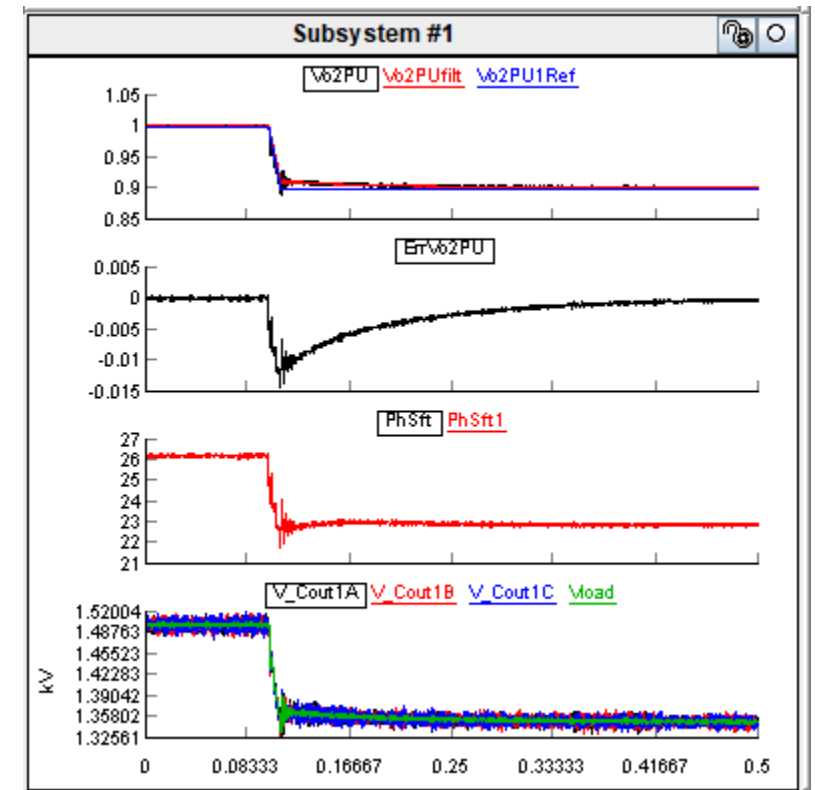

**DAB output voltage control loop**



# Conclusions & Future Plan



RTDS.COM

# Conclusion

- **DC Transformer simulation**
  - Implemented in SUBSTEP and GPES
  - Operation with good performance
  - Easily modify to different numbers of modules
  - Per-unitization control and draft variables usage

# Future Plan

- Release the developed control components to significantly simplify the implementation of DC Transformer Simulation
- Release simulation examples of DC Transformer in SUBSTEP and GPES simulation environment





RTDS.COM

THANK YOU!


QUESTIONS?





# Simulation in SUBSTEP
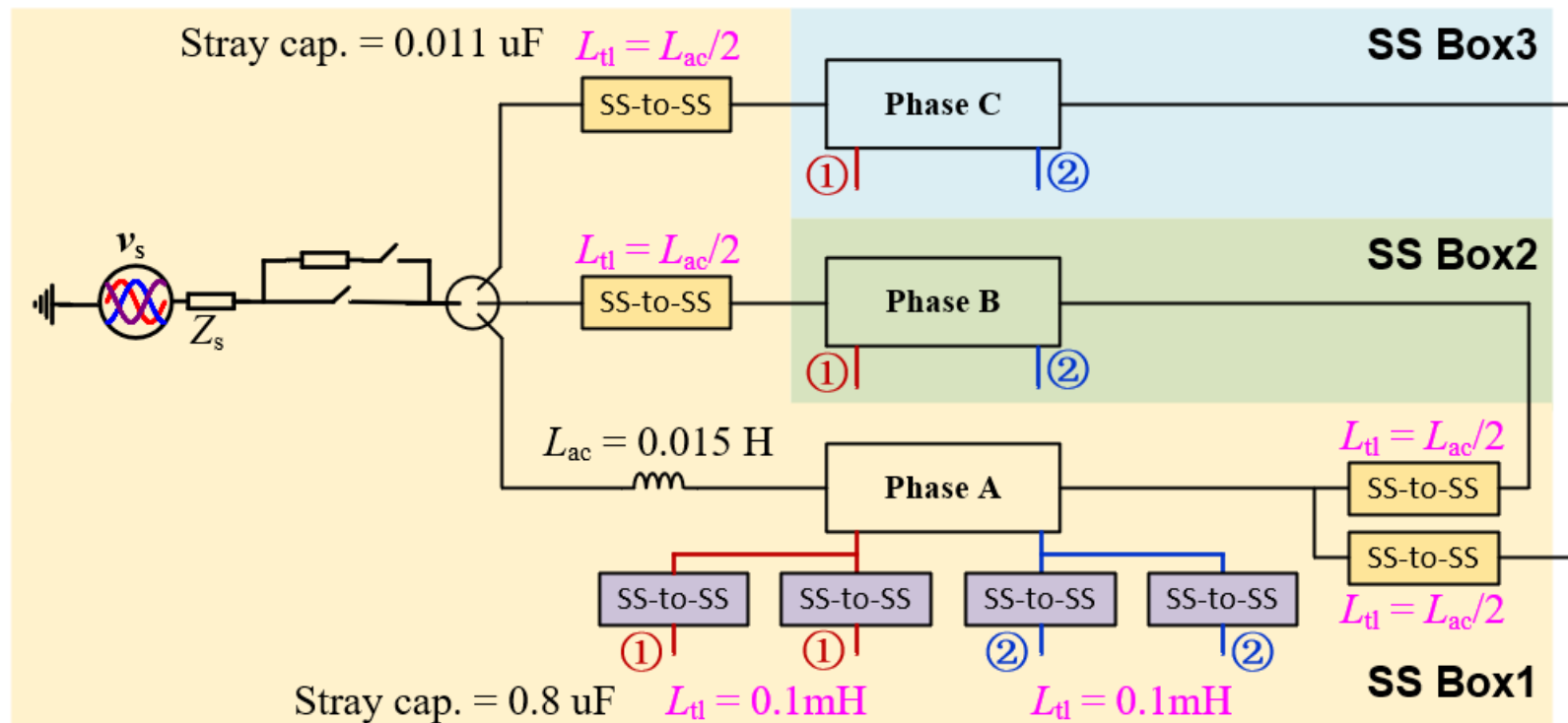
## Power circuit connection with interfaces








# One Phase Circuit in GPES Box

Each module: 17 branches, and 8 nodes

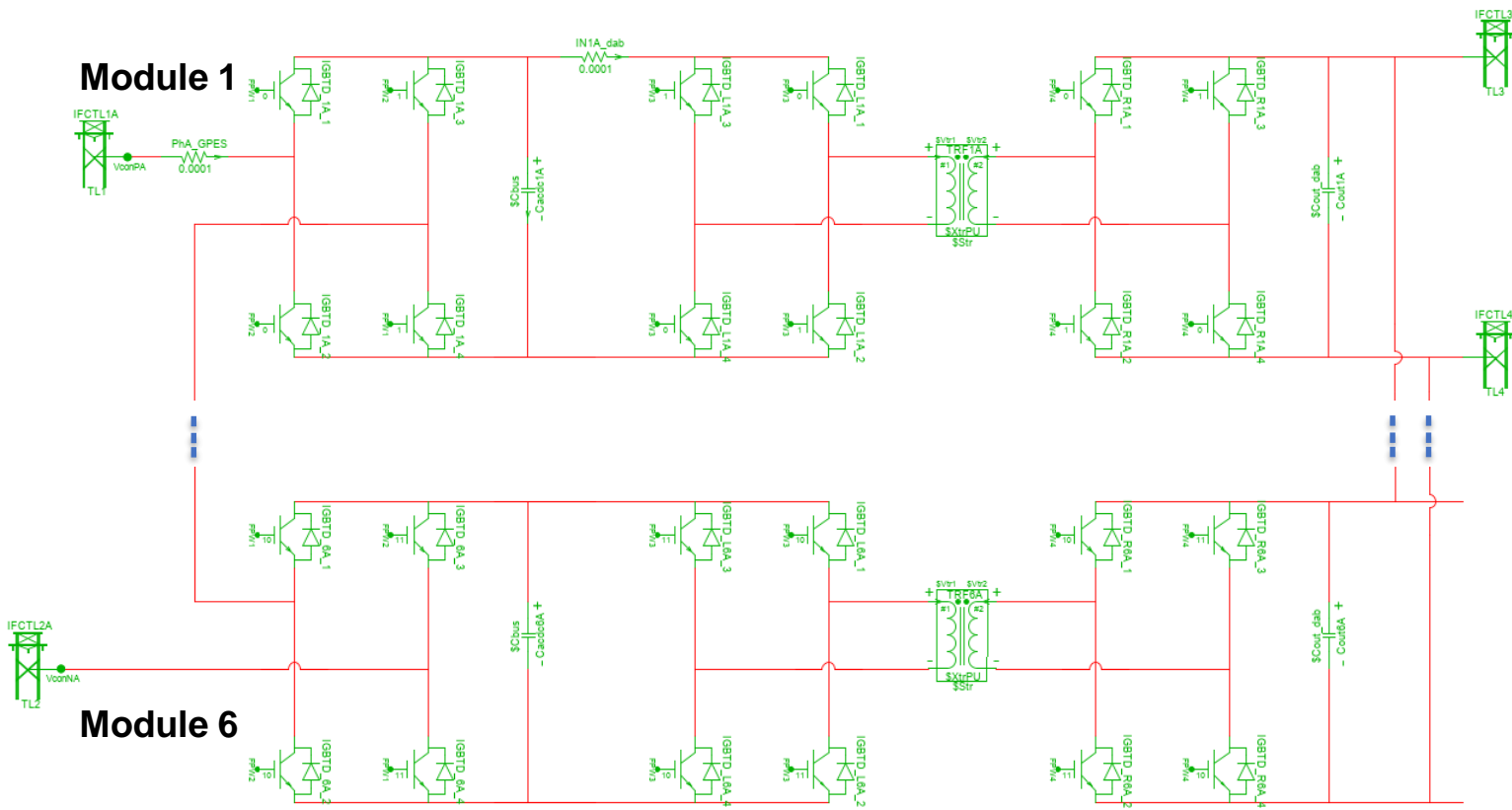

## Things to note:

- Transformer: base frequency equal to switching frequency
- Valve parameter for switches: *vswit*, *iswit* → (recommended to be equal to RMS/peak voltage and current in the valve)
- Interface: use the interface inductance as large as possible
- Simulation time step: as small as possible


## GPES environment.

- LC switching → artificial losses

## To reduce artificial losses:


- (1) Use small time step
- (2) Accurate *vswit* and *iswit*
- (3) Low switching frequency

# DAB Simulation Notes

 

**Transformer Base Frequency:**  
same as the switching frequency

rtds_ss_TRF S1PH.def					
SIGNAL MONITORING IN RT AND CC		SIGNAL NAMES		CORE ASSIGNMENT	
CONFIGURATION		SINGLE-PHASE TRANSFORMER PARAMETERS			
Name	Description	Value	Unit	Min	Max
vw1t	Rated Winding 1 RMS Voltage:	\$Vtr1	kV	0.001	
vw2t	Rated Winding 2 RMS Voltage:	\$Vtr2	kV	0.001	
MVA	Rated 1-Phase Transformer MVA:	\$Str	MVA	0.001	
frqt	Transformer Base Frequency:	\$fsw2	Hz	0.01	
rput	Total Winding Resistances:	0.0	pu	0.0	
xput	Total Winding Reactances:	\$XtrPU	pu	0.01	
mgls1	Winding 1 magnetizing losses:	0.00001	pu	0.00001	
mgls2	Winding 2 magnetizing losses:	0.00001	pu	0.00001	

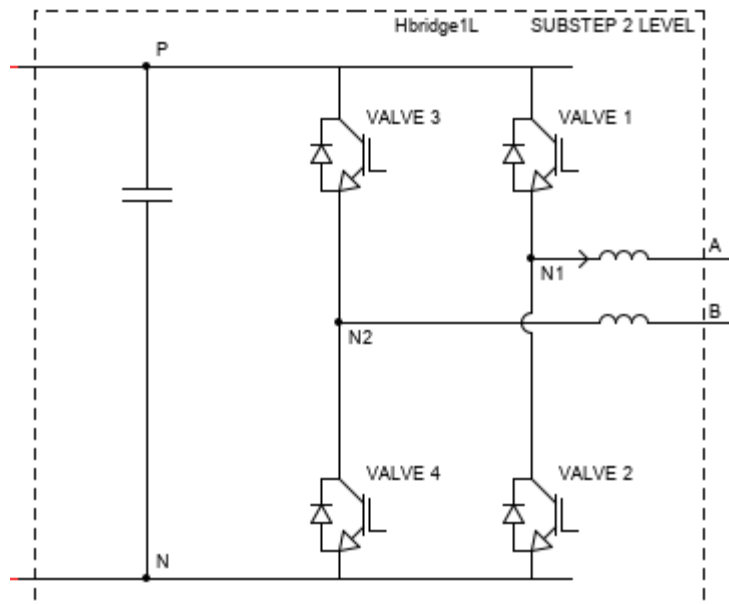

rtds_ss_LEV2_V3.def					
ENABLE MONITORING IN RUNTIME AND CC		SIGNAL NAMES		CORE ASSIGNMENT	
VALVE PARAMETERS		DC CAPACITOR PARAMETERS			
VALVE FIRING PULSES INPUT NAMES		AC REACTOR PARAMETERS			
VSC 2-LEVEL EMBEDDED BRIDGE CONFIGURATION					
Name	Description	Value	Unit	Min	Max
rvlon	Valve ON Resistance:	0.005	Ohms	0.0001	
rvlof	Valve OFF Resistance:	1.0e5	Ohms	1.0	
snbc	Snubber Series Capacitance:	\$Csnb1	MicroF	0.001	
snbr	Snubber Series Resistance:	\$Rsnb1	Ohms	1.0	


## VALVE PARAMETERS:

- rvlon, rvlof: used to simulate system losses
- snbc, snbr: used to suppress numerical oscillations → should be properly selected
- **Recommendations: snbc\*snbr = 2\*SubtimeStep, and snbr = 500 Ω to 2000 Ω**

# DAB Simulation Notes
 
## Substep to Substep Interface:

- Introduce 1 sub-timestep delay
- Stray capacitance:  $C = \text{sub-timestep}^2 / L_{tl}$
- $L_{tl}$ : Interface inductance



## Recommendations:

- Dividing large system through the branch with large inductance
- Put the interface inductance as large as possible
- Use simulation time step as small as possible

If_rtds_sharc_sld_TL16CAL					
PARAMETERS OF LINE WITH 1 SUBSTEP TRAVEL TIME					
CONFIGURATION		CORE ASSIGNMENT		DEBUG	
Name	Description	Value	Unit	Min	Max
local_nmcond	Number of conductors for 1 substep Tline	1		1	12
Lgrd	Inductance of Ground Mode of the line:	\$Lac2	Henries	1.0e-7	
Rgrd	Resistance of the Ground Mode of the line:	0.0	Ohms	0.0	
Laer	If No. of Cond. > 1, Inductance of Aerial Modes:	10.0e-7	Henries	1e-7	1e8
Raer	If No. of Cond. > 1, Resistance of Aerial Modes:	0.0	Ohms	0.0	1.0e8

Update Cancel Cancel All